

Qb. calculate the forward and reverse resistances offered by a Si diode at $I_F = 100\text{mA}$ + $V_R = 75\text{V}$, $V_R = 50\text{V}$ + $I_R = 100\text{nA}$.

Soln: At $I_F = 100\text{mA}$, for Si $V_F = 0.7\text{V}$
forward resistance $R_F = \frac{V_F}{I_F} = \frac{0.7}{100\text{mA}} = \underline{7\Omega}$


At $V_R = 50\text{V}$, $I_R = 100\text{nA}$,

reverse resistance $R_R = \frac{V_R}{I_R} = \frac{50\text{V}}{100\text{nA}} = \underline{500\text{M}\Omega}$

At $V_R = 75\text{V}$, $I_R = 100\text{nA}$,

$R_R = \frac{75\text{V}}{100\text{nA}} = \underline{750\text{M}\Omega}$

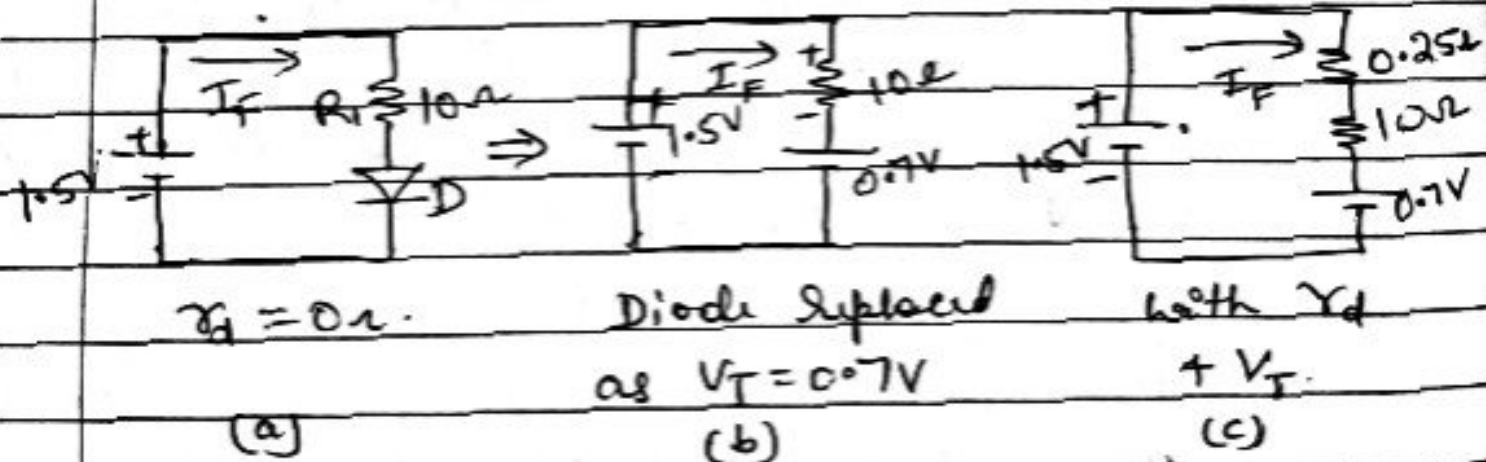Pb. Calculate I_F for the diode circuit assuming that the diode has $V_F = 0.7V$ and $r_d = 0$.
Recalculate current by taking $r_d = 0.25\Omega$



By applying KVL to (b),

$$V - I_F \times 10\Omega - 0.7V = 0.$$

$$\frac{1.5V - 0.7V}{10\Omega} = I_F = \underline{80mA}.$$

Applying KVL to (c)

$$V - I_F R_1 - I_F r_d - 0.7V = 0$$

$$\frac{1.5 - 0.7}{(0.25 + 10)} = I_F = \underline{78mA}$$


Reduction in diode current as resistance increases.

Date

--	--	--

Diode circuits numericals.

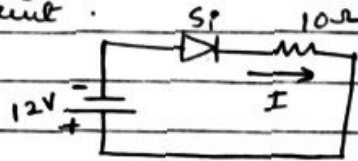1. Find the value of current I in the following circuit.




Sol. The Si diode is reverse biased by $-12V$.
So it does not conduct. $\therefore I = 0$.

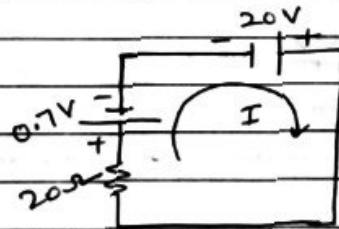2. Calculate the current I in the circuit.



Sol. Here 10Ω is independent of $20V$. Hence the equivalent circuit is




Applying KVL to the loop,

$$-0.7V + 20V - I \times 20\Omega = 0$$


$$\therefore I = \frac{20 - 0.7}{20} = 0.965A = \underline{965mA}$$

3. For the circuit calculate I & V_o .

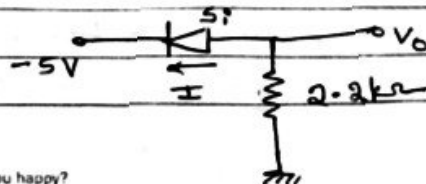

What makes you happy?

Sol. The equivalent circuit is

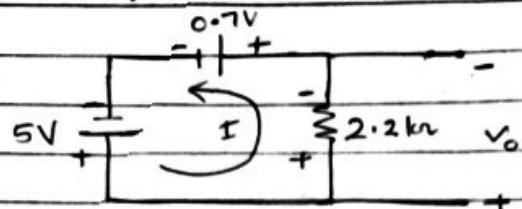


Applying KVL, we have

$$+5V - 2.2k\Omega \times I - 0.7V = 0$$


$$\therefore I = \frac{5 - 0.7}{2.2k\Omega} = \underline{1.95mA}$$

$$\begin{aligned} 4 \quad V_o &= 1.95mA \times 2.2k\Omega \\ &= \underline{4.3V} \end{aligned}$$

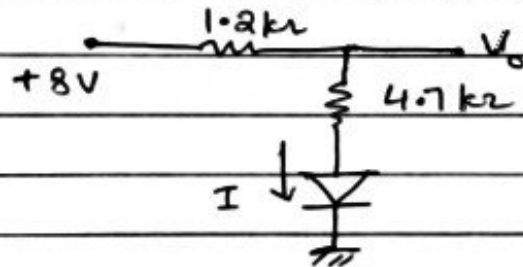4. Calculate I & V_o for the given circuit



sol. The equivalent circuit is shown as

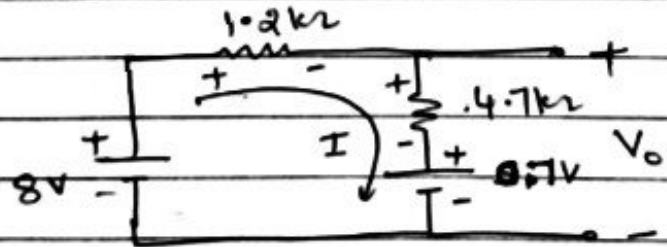

Applying KVL, we get

$$8V - I \times 1.2k - I \times 4.7k - 0.7V = 0$$

$$I = \frac{8 - 0.7}{(4.7 + 1.2)k} = 1.237mA$$

What makes you happy?

#

$$V_o = I \times 4.7 \times 10^3 + 0.7$$

$$= 1.237 \times 10^{-3} \times 4.7 \times 10^3 + 0.7$$


$$= \underline{6.51V}$$

Date


PNB

--	--	--

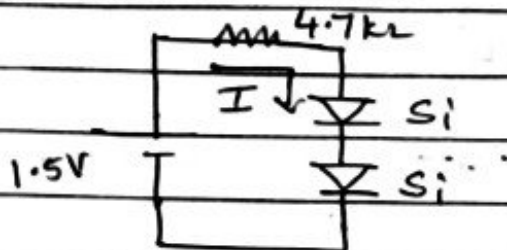5. Calculate the value of diode current I in the circuit below.



sol. The equivalent circuit is

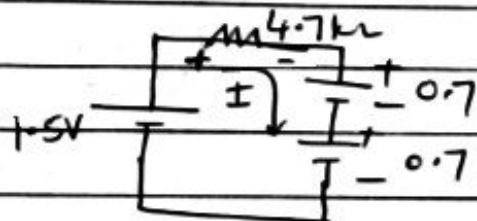


Applying KVL,


$$1.5V - 0.7V - 0.7V - I \times 4.7k = 0$$

$$I = \frac{1.5 - 1.4}{4.7k} = \underline{0.021mA}$$

6. Calculate I in the circuit.

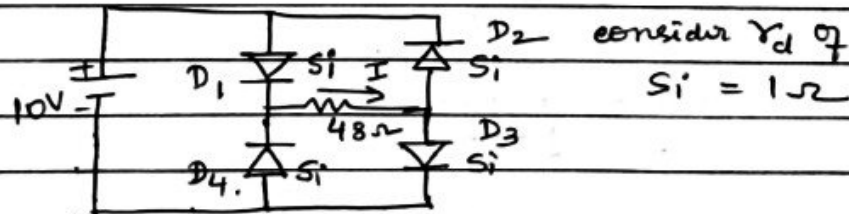

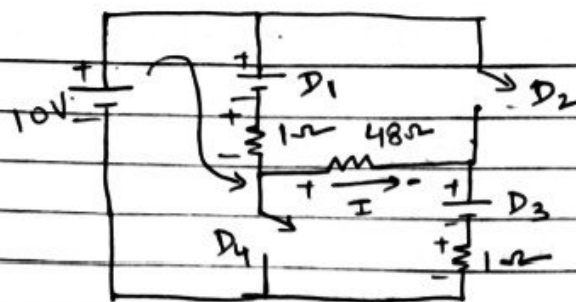soln In the circuit, for a supply of 10V, only diodes D_1 & D_3 gets forward biased. D_2 & D_4 are open switches. Equivalent circuit is as below.




Applying KVL. \therefore

$$10V - 0.7V - I(1\Omega + 48\Omega + 1\Omega) - 0.7V = 0$$

$$I = \frac{10V - 1.4V}{50\Omega} = 0.172A$$



$$= \underline{\underline{172mA}}$$

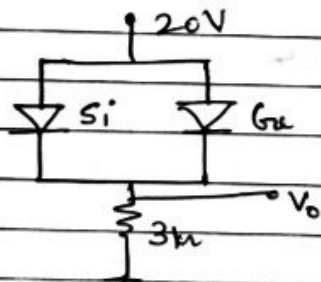8. Calculate the current in the circuit & V_o .



Here G_e gets forward biased first - once 20V is switched ON. S_i never gets to switch ON.

Equivalent ckt is

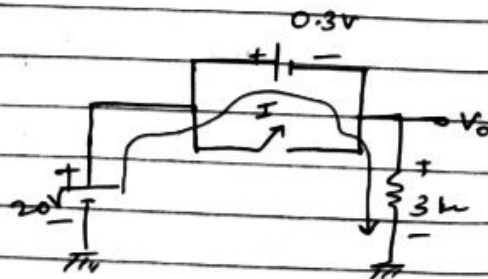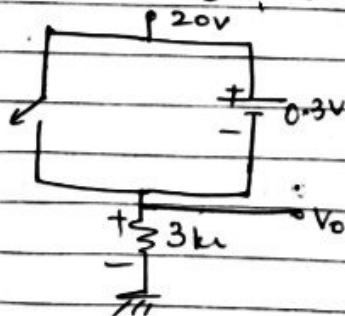

$$20 - 0.3 - I \times 3k\Omega = 0$$

$$\therefore I = \frac{20 - 0.3}{3k\Omega} = \underline{\underline{6.56mA}}$$

$$V_o = I \times 3k\Omega = \underline{\underline{19.7V}}$$

Rectifier circuits : Numericals.

1. A sinusoidal voltage of peak value 40V & frequency 50Hz is applied to a HWR without filter. It has a load $R_L = 800\Omega$ with $R_f = 8\Omega$. Calculate a) peak, dc and rms value of load current
b) Dc o/p power
c) Ac i/p power
d) Rectifier efficiency.

Soln. Given: $V_m = 40V$, $f = 50Hz$.
 $R_L = 800\Omega$, $R_f = 8\Omega$

a) Peak value of the load current I_m is

$$I_m = \frac{V_m}{R_L + R_f} = \frac{40}{800 + 8} = \underline{49.5mA}$$

$$I_{dc} = \frac{I_m}{\pi} = \frac{49.5mA}{\pi} = \underline{15.757mA}$$

$$I_{rms} = \frac{I_m}{2} = \frac{49.5mA}{2} = \underline{24.75mA}$$

b) Dc power to load. $P_{dc} = I_{dc}^2 R_L$

$$= (15.757 \times 10^{-3})^2 \times 800$$

$$= \underline{198.45mW}$$

c) Ac i/p power. $P_{ac} = I_{rms}^2 (R_L + R_f)$

$$= (24.75mA)^2 (800 + 8)$$

$$= 494.95mW$$

d) Efficiency $\eta = \frac{P_{dc}}{P_{ac}} = \frac{198.45mW}{494.95mW}$

$$= 0.4009$$

$$\therefore \eta = \underline{40.09\%}$$

2. An input to a HWR is $23 \sin 314t$. If $R_f = 50\Omega$ and $R_L = 500\Omega$ determine,

- i) DC load voltage ii) RMS load voltage
iii) Rectification efficiency iv) dc power delivered to the load.

Soln. Given $V_{in} = V_m \sin \omega t$
 $= 23 \sin 314t$

$$R_f = 50\Omega \quad R_L = 500\Omega$$

i) $V_{dc} = I_{dc} \times R_L$

$$I_{dc} = \frac{I_m}{\pi}, \quad I_m = \frac{V_m}{R_f + R_L} = \frac{23}{50 + 500}$$

$$= 41.81 \text{ mA}$$

$$\therefore I_{dc} = \frac{41.81 \text{ mA}}{\pi} = 13.31 \text{ mA}$$

$$\therefore V_{dc} = 13.31 \text{ mA} \times 500\Omega = 6.65 \text{ V}$$

ii) $V_{rms} = I_{rms} \times R_L$

$$I_{rms} = \frac{I_m}{2}, \quad I_m = \frac{V_m}{R_f + R_L}$$

$$= \frac{23}{550} = 41.81 \text{ mA}$$

$$I_{rms} = \frac{41.81 \text{ mA}}{2}$$

$$= 20.90 \text{ mA}$$

$$\therefore V_{rms} = 20.90 \text{ mA} \times 500\Omega$$

$$= 10.45 \text{ V}$$

iii) $P_{dc} = I_{dc}^2 \times R_L$

$$= (13.31 \text{ mA})^2 \times 500$$

$$= 88.57 \text{ mW}$$

iv) $\eta = \frac{0.406}{1 + R_f/R_L} = 36.91 \%$

3. In a Full wave bridge rectifier, the transformer secondary voltage is $100 \sin \omega t$. The forward resistance of each diode is 25Ω + load resistance is 950Ω . Calculate
 a) dc o/p V_g , b) Ripple factor c) Efficiency,

Solu. $V_g = V_m \sin \omega t = 100 \sin \omega t$

$V_m = 100$, $R_f = 25 \Omega$, $R_L = 950 \Omega$

a) $V_{dc} = I_{dc} R_L$

$I_{dc} = \frac{2I_m}{\pi}$, $I_m = \frac{V_m}{2R_f + R_L} = \frac{100}{2 \times 25 + 950}$

$I_m = \frac{100}{1000} = 100 \text{ mA}$

$\therefore I_{dc} = \frac{100 \text{ mA} \times 2}{\pi} = 63.66 \text{ mA}$

$V_{dc} = I_{dc} R_L = 63.66 \text{ mA} \times 950$
 $= 60.478 \text{ V}$

b) Ripple factor (r)

$I_{rms} = \frac{I_m}{\sqrt{2}}$

$r = \sqrt{\left(\frac{I_{rms}}{I_{dc}}\right)^2 - 1}$

$= \frac{100 \text{ mA}}{\sqrt{2}}$

$r = \sqrt{\left(\frac{70.71 \text{ mA}}{63.66 \text{ mA}}\right)^2 - 1} = \sqrt{1.233 - 1}$

$= 70.71 \text{ mA}$

$= \sqrt{0.2337} = 0.4834$

$\therefore r = 48.34\%$

$\therefore \eta = \frac{P_{dc}}{P_{ac}} = \frac{I_{dc}^2 R_L}{I_{rms}^2 (2R_f + R_L)} = \frac{3.85}{5 \times 10^{-3} (1000)}$
 $= 0.77$

$\eta = 77\%$

4. A bridge rectifier uses 4 diodes with rms voltage of 110V. Forward resistance of each diode is 25Ω with load R_L of $1k\Omega$. Find i) max value of current ii) DC value of current through the load iii) DC load voltage.

Soln: given $V_{rms} = 110V$, $R_f = 25\Omega$, $R_L = 1k\Omega$

$$V_{rms} = \frac{V_m}{\sqrt{2}} \therefore V_m = V_{rms} \times \sqrt{2} = 155.56V$$

$$i) I_m = \frac{V_m}{2R_f + R_L} = \frac{155.56}{50 + 1 \times 1000} = \underline{148.15mA}$$

$$ii) I_{dc} = \frac{2I_m}{\pi} = \frac{2 \times 148.15mA}{\pi} = \underline{94.36mA}$$

$$iii) V_{dc} = I_{dc} \times R_L = 94.36mA \times 1k\Omega = \underline{94.36V}$$

with capacitor filter

Date

PNB

1. Determine the ripple factor of a bridge rectifier using a capacitor filter. The load used is $2\text{ k}\Omega$ while dc o/p V_g is 12 V . Assume supply frequency of 50 Hz and ideal diodes. The capacitor of $100\text{ }\mu\text{F}$ is used in the filter circuit.

Solu. given: $R_L = 2\text{ k}\Omega$, $V_{dc} = 12\text{ V}$, $f = 50\text{ Hz}$,
ideal diodes, $C = 100\text{ }\mu\text{F}$

$$\gamma = \frac{1}{4\sqrt{3} f C R_L} = \frac{1}{4\sqrt{3} \times 50 \times 2 \times 10^3 \times 100 \times 10^{-6}}$$
$$= \frac{1}{69.28} = 0.0144$$

$$\% \gamma = \underline{\underline{1.44\%}}$$

2. Calculate the value of capacitor C that has to be used for filter of a Bridge rectifier to get a ripple factor of 0.01 . The rectifier supplies current to a load of $2\text{ k}\Omega$ while the supply frequency is 50 Hz .

Solu. given $\gamma = 0.01$ (1%), $R_L = 2\text{ k}\Omega$, $f = 50\text{ Hz}$.

$$\gamma = \frac{1}{4\sqrt{3} f C R_L} \therefore C = \frac{1}{4\sqrt{3} f R_L \gamma}$$
$$C = \frac{1}{4\sqrt{3} \times 50 \times 2 \times 10^3 \times 0.01} = \frac{1}{6928.203}$$
$$= 0.0001443$$


$$= \underline{\underline{144.34\text{ }\mu\text{F}}}$$

Numericals.

Date

1. A 24V, 600mW zener diode is used for providing a 24V stabilized supply to a variable load from a 32V supply. Calculate
 - i) Value of series resistance required
 - ii) Zener current when the load is 1200Ω.

Sol: Circuit diagram:

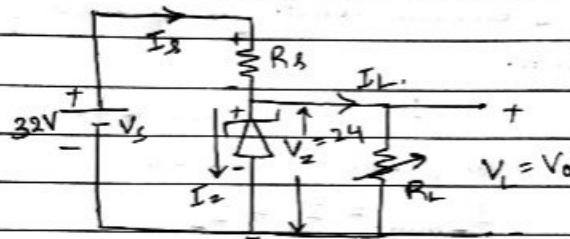

Given: $V_z = 24V$, $P_z = 600mW$, $V_s = 32V$.

- i) Without load R_L i.e. $I_L = 0$ for $R_L = 0$.
We know that $I_s = I_z + I_L$. (from the ckt)
Since $I_L = 0$, $I_s = I_z \text{ max.}$

$$P_z = I_z V_z.$$

$$\therefore I_z = \frac{P_z}{V_z} = \frac{600mW}{24V} = 25mA = I_{z \text{ max}}$$

Applying KVL,

$$I_s = I_{z \text{ max}} = 25mA$$

$$V_s - I_s R_s - V_z = 0.$$

$$32 - 25mA \times R_s - 24 = 0$$

$$\therefore R_s = \frac{32V - 24V}{25mA} = \underline{\underline{320\Omega}}$$

The value of series resistance to be connected in the circuit is $R_s = \underline{\underline{320\Omega}}$

What makes you happy?

PNB

Date

- ii) With load R_L :

$$\text{Wkt } I_s = I_L + I_z.$$

$$\text{also } V_s = V_o = V_L = I_L R_L$$

$$\Rightarrow V_z = I_L R_L.$$

Given $V_z = 24V$ & $R_L = 1200\Omega$.


$$\therefore I_L = \frac{V_z}{R_L} = \frac{24V}{1200\Omega} = \underline{\underline{20mA}}$$

Load current through a load of 1200Ω is 20mA.

\therefore At maximum load of 1200Ω, minimum zener current is

$$\begin{aligned} I_{z \text{ min}} &= I_s - I_L \\ &= 25mA - 20mA = \underline{\underline{5mA}} \end{aligned}$$

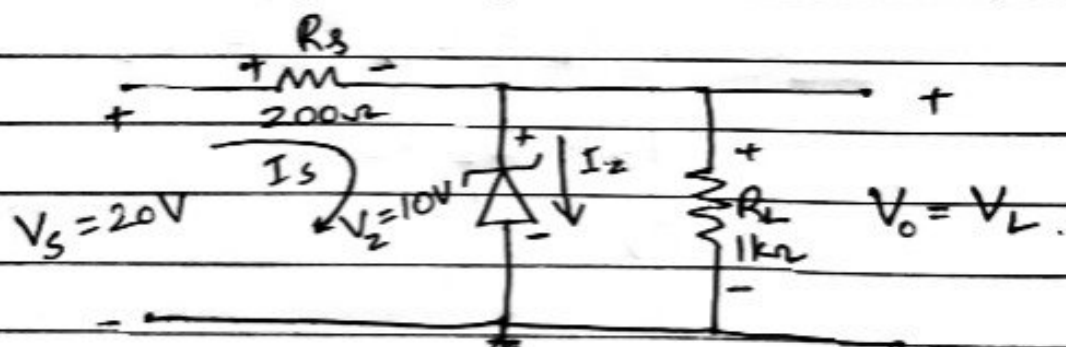2. A circuit has a Zener diode connected a/c the load with following details. Find I_s, I_L & P_z .



soln

Given, $V_s = 20V$, $R_s = 200\Omega$, $V_z = 10V$, $R_L = 1k\Omega$.
To find I_s, I_L and Power P_z .

Applying KVL to the i/p loop, we get

$$V_s - I_s R_s - V_z = 0.$$

$$20V - I_s \times 200\Omega - 10V = 0.$$

$$\therefore I_s = \frac{20V - 10V}{200\Omega} = \underline{\underline{50mA}}$$

Wkt $V_L = V_o = I_L R_L = V_z$.

$$\Rightarrow V_z = I_L R_L.$$

$$\therefore I_L = \frac{V_z}{R_L} = \frac{10V}{1 \times 10^3} = \underline{\underline{10mA}}$$

The load current through a load of $1k\Omega$ is 10mA

To find the current through Zener & hence the power dissipation.

Wkt $I_s = I_z + I_L$

$$\therefore I_z = I_s - I_L$$


$$= 50mA - 10mA = \underline{\underline{40mA}}$$

\therefore The power dissipated is

$$P_z = V_z I_z.$$

$$= 10V \times 40mA = \underline{\underline{400mW}}$$

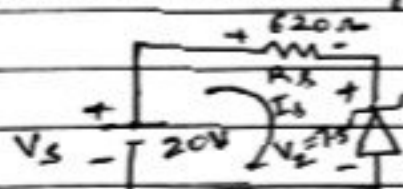3. A circuit uses a zener with $V_z = 7.5V$. Find the diode current and max power dissipation in the absence of load.



Given: $V_s = 20V$

$V_z = 7.5V$

$R_s = 620\Omega$

to find P_z with $R_L = 0$.

Sol. Wkt $I_s = I_R + I_z$.

since $R_L = 0$, $I_s = I_z \text{ max.}$

Applying KVL,

$$V_s - I_s R_s - V_z = 0.$$

$$20 - I_s \times 620 - 7.5 = 0.$$

$$\therefore I_s = I_z = \frac{20V - 7.5V}{620\Omega} = \underline{20.16mA}$$

\therefore Max zener current $I_{z\text{max}} = \underline{20.16mA}$

Power dissipation in zener is

$$P_z = I_z V_z$$

$$= 20.16mA \times 7.5V$$

$$= \underline{151.2mW}$$

PNS

Date

--	--

Numericals.

1. Calculate I_C & I_E for a transistor that has $\alpha = 0.98$ and $I_B = 100 \mu A$. Determine the value of β for the transistor.

Soln: Given $\alpha = 0.98$, $I_B = 100 \mu A$.

$$I_E = I_C + I_B.$$

$$I_C = \beta I_B.$$

$$\therefore \beta = \frac{\alpha}{1-\alpha} = \frac{0.98}{1-0.98} = \underline{49}.$$

$$I_C = \beta I_B \Rightarrow 49 \times 100 \times 10^{-6} A = 4.9 \times 10^{-3} A \\ = \underline{4.9 mA}$$

$$\& I_E = 4.9 \times 10^{-3} + 100 \times 10^{-6} \\ = \underline{5 mA}$$

2. Calculate α and β for $I_C = 1 mA$ and $I_B = 25 \mu A$. Determine the new base current to give $I_C = 5 mA$.

Soln:
$$\beta = \frac{I_C}{I_B} = \frac{1 mA}{25 \mu A} = \underline{40}$$

$$I_E = I_C + I_B = 1 mA + 25 \mu A = \underline{1.025 mA}$$

$$\alpha = \frac{I_C}{I_E} = \frac{1 mA}{1.025 mA} = \underline{0.976}$$

$$I_{B_{new}} = \frac{I_C}{\beta} = \frac{5 mA}{40} = \underline{125 \mu A}$$

3. Determine β and I_E for transistor where

Scanned by CamScanner

Date

P	N	B

$$I_B = 50 \mu A \text{ and } I_C = 3.65 \text{ mA}$$

Sol: $I_B = 50 \mu A$, $I_C = 3.65 \text{ mA}$ - given

$$I_E = I_B + I_C \Rightarrow 50 \mu A + 3.65 \text{ mA} \\ = \underline{\underline{3.70 \text{ mA}}}$$

$$\beta = \frac{I_C}{I_B} = \frac{3.65 \text{ mA}}{50 \mu A} = \underline{\underline{73}}$$

4. A transistor has $I_C = 3 \text{ mA}$ and $I_E = 3.03 \text{ mA}$. Find β of the transistor used. Assuming no change in the base current, find the new collector current when transistor is replaced with a new one with β of 70.

Sol: given, $I_C = 3 \text{ mA}$, $I_E = 3.03 \text{ mA}$

$$I_B = I_E - I_C \\ = 0.03 \text{ mA} = \underline{\underline{30 \mu A}}$$

$$\beta = \frac{I_C}{I_B} = \frac{3 \text{ mA}}{30 \mu A} = \underline{\underline{100}}$$

New collector current when transistor is replaced with $\beta = 70$ is

$$I_C = \beta I_B \Rightarrow 70 \times 30 \times 10^{-6} \\ I_C = \underline{\underline{2.1 \text{ mA}}}$$

5. Find I_c & I_E for a transistor with $\alpha = 0.99$ & $I_B = 20 \mu A$.

Sol: Given $\alpha = 0.99$ $I_B = 20 \mu A$.

$$\text{Wkt } I_c = \beta I_B \\ = \frac{\alpha}{1-\alpha} \cdot I_B$$

Scanned by CamScanner

PNB
Date

--	--	--

$$I_c = \frac{0.99}{1-0.99} (20 \times 10^{-6})$$

$$= \underline{1.98 \text{ mA}}$$

$$I_E = I_c + I_B = (1.98 + 0.02) \text{ mA}$$

$$I_E = \underline{\underline{2 \text{ mA}}}$$