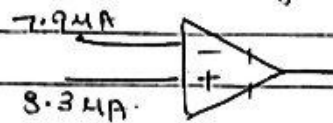


Numericals:

1. Determine the input bias current and input offset current I_B & I_{io} to an OPAMP if the current into noninverting terminal is $8.3 \mu A$ & inverting terminal is $7.9 \mu A$.



$$I_B = \frac{I_{B1} + I_{B2}}{2} = \frac{8.3 \mu A + 7.9 \mu A}{2} = 8.1 \mu A$$

$$I_{io} = |I_{B1} - I_{B2}| = |8.3 \mu A - 7.9 \mu A| = 0.4 \mu A$$

2. A certain OPAMP has a differential voltage gain of 1,00,000 and common mode gain of $A_c = 0.25$. Determine CMRR & express it in dB.

$$\text{given } A_d = 1,00,000$$

$$A_c = 0.25$$

$$CMRR = \frac{A_d}{A_c} = \frac{1,00,000}{0.25} = 4,00,000$$

$$\text{in dB, } CMRR|_{dB} = 20 \log_{10} (4,00,000) = 112.04 \text{ dB}$$

3. An OPAMP has a differential voltage gain of 2,500 and a CMRR of 30,000.

i) Determine common mode gain A_c

ii) Express CMRR in dB

$$\text{given } A_d = 2500 \quad CMRR = 30,000$$

$$i) \quad CMRR = \frac{A_d}{A_c}$$

$$\therefore A_c = \frac{A_d}{CMRR} = \frac{2500}{30,000} = 0.083$$

$$ii) \quad CMRR \text{ in dB} = 20 \log_{10} (30,000) = 89.54 \text{ dB}$$

4. An OP Amp has a common mode input signal of 3.2V to both the input terminals. This results in an o/p signal of 26mV . Determine common mode gain A_c & CMRR in dB. given that the differential gain is 100.

$$\text{given } V_c = 3.2\text{V}, V_o = 26\text{mV}$$

$$A_c = \frac{V_o}{V_c} = \frac{26\text{mV}}{3.2\text{V}} = \underline{\underline{0.0081}}$$

$$\text{CMRR} = \frac{A_d}{A_c} = \frac{100}{0.0081} = \underline{\underline{12345.6}}$$

$$\begin{aligned} \therefore \text{CMRR} |_{\text{dB}} &= 20 \log_{10} (12345.6) \\ &= \underline{\underline{81.83 \text{ dB}}} \end{aligned}$$

4. In a Colpitts oscillator, $C_1 = 100 \text{ pF}$, $C_2 = 260 \text{ pF}$. Find the value of L if the frequency of oscillations is 40 kHz .

Solu. Given: $C_1 = 100 \text{ pF}$ $C_2 = 260 \text{ pF}$.
 $L = ?$ $f = 40 \text{ kHz}$.

$$f = \frac{1}{2\pi \sqrt{L C_{eq}}} \quad C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

$$C_{eq} = \frac{100 \times 10^{-12} \times 260 \times 10^{-12}}{100 \times 10^{-12} + 260 \times 10^{-12}} = \underline{\underline{37.5 \text{ pF}}}$$

To find L . Square both sides of f .

$$f^2 = \frac{1}{4\pi^2 L C_{eq}}$$

$$\therefore L = \frac{1}{4\pi^2 f^2 C_{eq}}$$

$$= \frac{1}{4\pi^2 (40 \times 10^3)^2 (37.5 \times 10^{-12})}$$

$$\therefore L = \underline{\underline{0.422 \text{ H}}}$$

5. In a Colpitts oscillator, $L = 5\text{mH}$. Find C_1 and C_2 if the frequency of oscillations is $f = 50\text{kHz}$. Assume a feedback factor of $\beta = 10\%$.

Scanned by CamScanner

Soln $L = 5\text{mH}$. $f = 50\text{kHz}$. $\beta = 10\% = 0.1$

$$f = \frac{1}{2\pi \sqrt{L C_{eq}}}$$

$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

Squaring f ,

$$f^2 = \frac{1}{4\pi^2 L C_{eq}}$$

$$C_{eq} = \frac{1}{4\pi^2 L f^2} = \frac{1}{4\pi^2 \times 5 \times 10^{-3} \times (50 \times 10^3)^2}$$

$$C_{eq} = 2.02\text{nF}$$

Wkt $C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$, $\beta = 0.1 = \frac{C_2}{C_1}$

$$\therefore C_2 = 0.1 C_1$$

$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2} = \frac{C_1 \times 0.1 C_1}{1.1 C_1} = \frac{0.1 C_1}{1.1}$$

$$\Rightarrow C_{eq} = \frac{0.1 C_1}{1.1}$$

$$2.02\text{nF} = \frac{0.1 C_1}{1.1}$$

$$\therefore C_1 = 22.22\text{nF}$$

$$\begin{aligned} \& C_2 &= 0.1 \times 22.22\text{nF} \\ &= 2.222\text{nF} \end{aligned}$$

5. Design a Colpitts oscillator whose frequency of oscillation is 40 kHz , $L = 10\text{ mH}$ and $C_1 = C_2 = C$.

Soln. $C_1 = C_2 = C$, $f = 40\text{ kHz}$, $L = 10\text{ mH}$.

$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2} = \frac{C^2}{2C} = \frac{C}{2}.$$

$$\therefore f = \frac{1}{2\pi\sqrt{C_{eq}L}} \quad \text{Squaring +,}$$

$$f^2 = \frac{1}{4\pi^2 C_{eq} L}.$$

$$C_{eq} = \frac{1}{4\pi^2 L f^2}.$$

$$\frac{C}{2} = \frac{1}{4\pi^2 (40 \times 10^3)^2 \times 10 \times 10^{-3}}$$

$$\therefore C = 3.166\text{ nF}.$$

$$C_1 = C_2 = \underline{\underline{3.166\text{ nF}}}$$

1. An inverting amplifier has $R_1 = 1\text{ k}\Omega$ and $R_f = 20\text{ k}\Omega$. Calculate the gain A .

Sol. Given $R_1 = 1\text{ k}\Omega$ $R_f = 20\text{ k}\Omega$

$$\therefore A = -\frac{R_f}{R_1} = -\frac{20\text{ k}\Omega}{1\text{ k}\Omega} = -20$$

2. An OP-Amp in inverting configuration has a gain of $+40$. If the applied i/p voltage is 3 mV what is V_o ?

Sol. given $A = +40$

$$V_i = 3\text{ mV}$$

$$\therefore V_o = -\frac{R_f}{R_1} V_i = -A V_i$$

$$\therefore V_o = -40 (3\text{ mV})$$

$$V_o = -120\text{ mV}$$

3. Design an inverting amplifier with a gain of -50 and a $2\text{ k}\Omega$ resistance R_1 . Draw the circuit fig.


Sol. given $R_1 = 2\text{ k}\Omega$ $A = -50$

To calculate feedback resistor R_f .

Wkt $A = -\frac{R_f}{R_1}$ for inverting amplifier.

$$\therefore -50 = -\frac{R_f}{2\text{ k}\Omega}$$

$$\Rightarrow R_f = 100\text{ k}\Omega$$

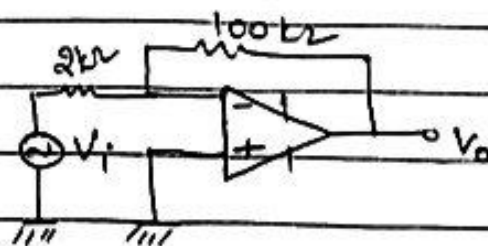


4. A sine wave of $0.5V$ peak value is applied as an i/p to an inverting amplifier with $R_i = 10k\Omega$ and $R_f = 50k\Omega$. It uses a power supply of $\pm 12V$. Determine the output voltage and sketch i/p & o/p waveforms. If now an i/p voltage of $5V$ peak is applied, what is the o/p. Sketch the waveforms.

Soln given $V_i = 0.5V_p$, $R_i = 10k\Omega$, $R_f = 50k\Omega$
It gives an o/p voltage for a supply of $\pm 12V$. So $V_o = ?$

Wkt $V_o = -\frac{R_f}{R_i} V_i = -\frac{50k\Omega}{10k\Omega} V_i = -5(0.5V_p)$

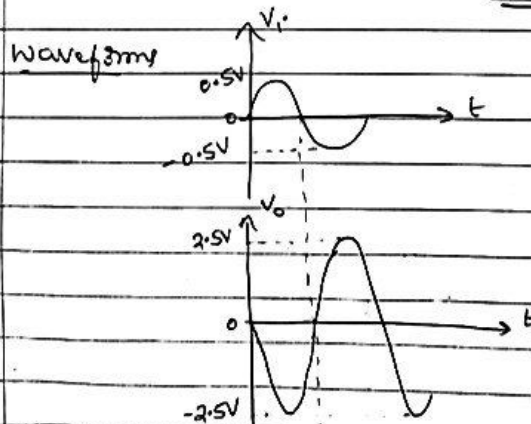$\therefore V_o = -2.5V_p$ or $-5V_{p-p}$



- (1) If a $5V_p$ is applied as i/p voltage $V_o = ?$


Scanned by CamScanner

Date P N B

$V_o = -\frac{R_f}{R_i} V_i = -5 \times 5V_p$
 $= -25V_p$ or $-50V_{p-p}$

But given $+V_{cc}$ & $-V_{cc}$ supplies as $\pm 12V$.
Hence the o/p voltage will saturate at $\pm 12V$.
(The peak levels get clipped off after $\pm 12V$).

Waveforms

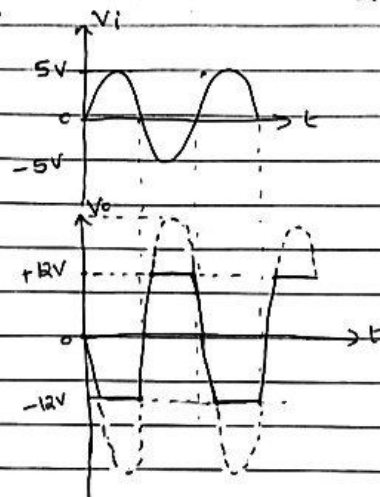

5. In a non-inverting amplifier using OP-Amp, $R_1 = 2k\Omega$, $R_f = 200k\Omega$. Supply voltages are $\pm 15V$. calculate V_o if the applied i/p voltage is $1.5V_{pp}$

sol: given: $R_1 = 2k\Omega$, $R_f = 200k\Omega$,
 $\pm V_{CC}, -V_{EE} = \pm 15V$.


$$V_o = \left(1 + \frac{R_f}{R_1}\right) V_i$$

Scanned by CamScanner


$$V_o = \left(1 + \frac{200k\Omega}{2k\Omega}\right) 1.5V_{pp}$$
$$= \underline{\underline{151.5V_{p-p}}}$$

given $V_i = 1.5V_{pp}$ with $\pm 15V$ supply voltages.
Op will saturate at $\pm 15V$.

waveform

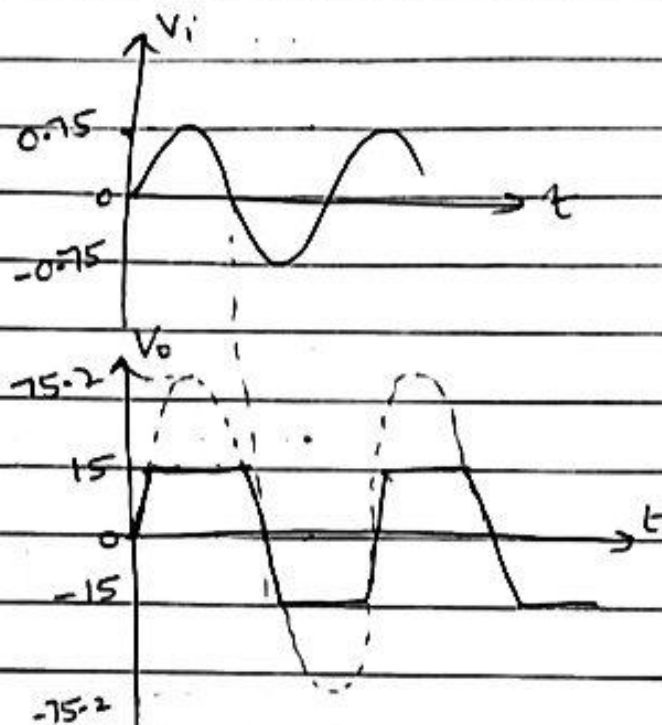

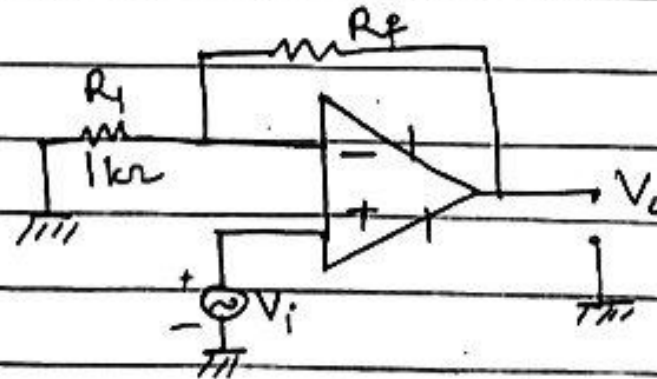6. For an OP-Amp circuit shown in figure below gain is 60. $R_1 = 1k\Omega$ what is R_f ?



It is a non inverting amplifier circuit.

Hence
$$V_o = \left(1 + \frac{R_f}{R_1}\right) V_i$$

Scanned by CamScanner

Date

	P	N	B
--	---	---	---

where closed loop gain

$$A = 1 + \frac{R_f}{R_1} \quad \text{Given } A = 60$$

$$60 = 1 + \frac{R_f}{1k}$$

$$\therefore \frac{R_f}{1k} = 59$$

$$\text{or } R_f = 59 \times 1k$$

$$R_f = \underline{\underline{59k\Omega}}$$

Date PNB

where closed loop gain

$$A = 1 + \frac{R_f}{R_1} \quad \text{given } A = 6.$$

$$60 = 1 + \frac{R_f}{1k}$$


$$\therefore \frac{R_f}{1k} = 59$$

$$\text{or } R_f = 59 \times 1k$$

$$R_f = \underline{\underline{59k\Omega}}$$

Inverting Summer.

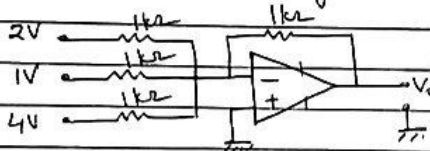7. In the circuit figure of an inverting summer determine the o/p voltage.



soln: o/p voltage of an inverting summer

$$\text{is } V_o = - \left(\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right)$$

$$\text{Since } R_f = R_1 = R_2 = R_3 = 1k\Omega,$$

$$V_o = - (2V + 1V + 4V)$$

$$= \underline{\underline{-7V}}$$

For the same circuit if $R_1 = 2k\Omega$, $R_2 = 1k\Omega$
 $\& R_3 = 4k\Omega$, $R_f = 20k\Omega$, $V_o = ?$

Scanned by CamScanner

Date PNB

$$V_o = - \left(\frac{20k\Omega}{2k\Omega} + 1 \frac{20k\Omega}{1k\Omega} + 4 \frac{20k\Omega}{4k\Omega} \right)$$

$$= - (20 + 20 + 20)$$

$$= \underline{\underline{-60V}}$$

8. Design an inverting summer using OP-Amp to give an o/p voltage $V_o = -(3V_1 + 4V_2 + 5V_3)$ with $R_f = 120k\Omega$.

soln: For an inverting summer,

$$V_o = - \left(\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right) \quad \text{--- (1)}$$

$$R_f = 120k\Omega.$$

$$\text{given } V_o = -(3V_1 + 4V_2 + 5V_3) \quad \text{--- (2)}$$


equating (1) & (2),

$$\frac{R_f}{R_1} = 3 \Rightarrow \frac{120k}{3} = R_1 = \underline{\underline{40k\Omega}}$$

$$\frac{R_f}{R_2} = 4 \Rightarrow \frac{120k}{4} = R_2 = \underline{\underline{30k\Omega}}$$

Inverting Summer.

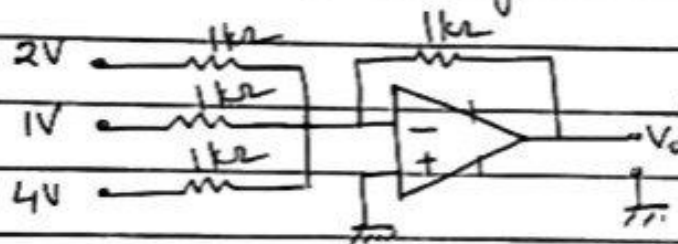7. In the circuit figure of an inverting summer determine the o/p voltage.



Soln: o/p voltage of an inverting summer is

$$V_o = - \left(\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right)$$

Since $R_f = R_1 = R_2 = R_3 = 1k\Omega$,

$$\begin{aligned} V_o &= - (2V + 1V + 4V) \\ &= - \underline{7V} \end{aligned}$$

For the same circuit if $R_1 = 2k\Omega$, $R_2 = 1k\Omega$ & $R_3 = 4k\Omega$, $R_f = 20k\Omega$, $V_o = ?$

Scanned by CamScanner

$$\begin{aligned} V_o &= - \left(\frac{20k\Omega}{2k\Omega} + 1 \frac{20k\Omega}{1k\Omega} + 4 \frac{20k\Omega}{4k\Omega} \right) \\ &= - (20 + 20 + 20) \\ &= - \underline{60V} \end{aligned}$$

Date PNB

8. Design an inverting summer using OP-Amp to give an o/p voltage $V_o = -(3V_1 + 4V_2 + 5V_3)$ with $R_f = 120k$.

Soln: For an inverting summer,

$$V_o = -\left(\frac{R_f}{R_1}V_1 + \frac{R_f}{R_2}V_2 + \frac{R_f}{R_3}V_3\right) \quad - (1)$$

$$R_f = 120k.$$


$$\text{given } V_o = -(3V_1 + 4V_2 + 5V_3) \quad - (2)$$

equating (1) & (2),

$$\frac{R_f}{R_1} = 3 \Rightarrow \frac{120k}{3} = R_1 = \underline{40k}$$

$$\frac{R_f}{R_2} = 4 \Rightarrow \frac{120k}{4} = R_2 = \underline{30k}$$
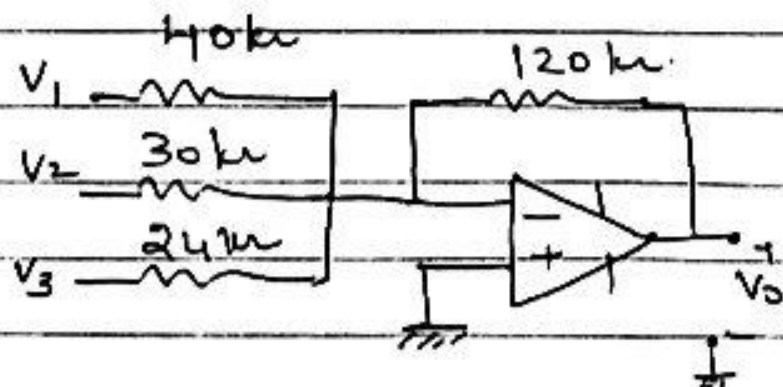
$$\frac{R_f}{R_3} = 5 \Rightarrow \frac{120k}{5} = R_3 = \underline{24k}$$



9. Design an inverting summer for
 $V_o = 0.2V_1 + 1V_2 + 4V_3$ with $R_f = 20k\Omega$

Scanned by CamScanner

Date PMT

Soln : Output voltage for an inverting summer is

$$V_o = - \left(\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right) \quad (1)$$

Given $V_o = 0.2V_1 + 1V_2 + 4V_3$.


$$\text{ie } V_o = - (0.2(-V_1) + 1(-V_2) + 4(-V_3)) \quad (2)$$

Comparing (1) & (2)

$$\frac{R_f}{R_1} = 0.2 \Rightarrow \frac{20k\Omega}{0.2} = R_1 = \underline{100k\Omega}$$

$$\frac{R_f}{R_2} = 1 \Rightarrow \frac{20k\Omega}{1} = R_2 = \underline{20k\Omega}$$
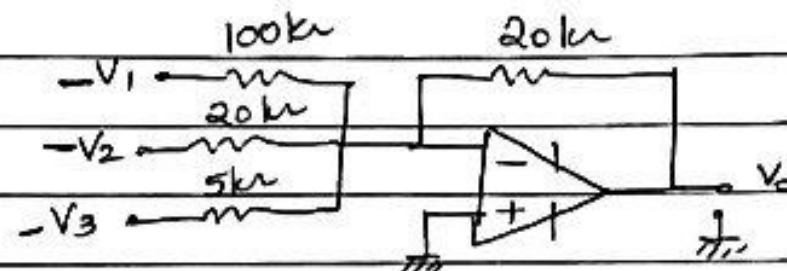
$$\frac{R_f}{R_3} = 4 \Rightarrow \frac{20k\Omega}{4} = R_3 = \underline{5k\Omega}$$



Numericals on IC 555 timer.

10. For an IC 555 timer to work in astable mode the components considered are $R_1 = 1k\Omega$, $R_2 = 10k\Omega$ with $C = 0.01\mu F$. What is the frequency of oscillations generated? Duty cycle?

Sol. Given $R_1 = 1k\Omega$, $R_2 = 10k\Omega$, $C = 0.01\mu F$.

$$f = \frac{1}{T}, \quad T = T_{ON} + T_{OFF}$$

$$\begin{aligned} T_{ON} &= 0.693 (R_1 + R_2) C \\ &= 0.693 (1k\Omega + 10k\Omega) 0.01\mu F \\ &= 0.693 (11k\Omega) 0.01\mu F \end{aligned}$$

What makes you happy?

Scanned by CamScanner

Date

P	NB	
---	----	--

$$= 0.693 (11 \times 10^3 \times 0.01 \times 10^{-6})$$

$$= 0.693 (11 \times 0.01 \times 10^{-3})$$

$$T_{ON} = \underline{76.23 \mu s}$$

$$T_{OFF} = 0.693 R_2 C = 0.693 \times 10k\Omega \times 0.01\mu F$$

$$= 0.693 \times 10 \times 10^3 \times 0.01 \times 10^{-6}$$

$$= 0.0693 \times 10^{-3}$$

$$= \underline{69.3 \times 10^{-6} s}$$

$$\therefore T = 145.53 \mu s$$

$$f = \underline{6.871 kHz}$$

$$(f = \frac{1}{T})$$

$$\text{Duty cycle} = \frac{T_{ON}}{T} = \frac{76.23 \mu s}{145.53 \mu s}$$

$$= 0.5238$$

$$\therefore D = \underline{52.38 \%}$$

11. A 555 timer IC has $R_1 = 4\text{ k}\Omega$, $R_2 = 4\text{ k}\Omega$,
 $C = 0.01\text{ }\mu\text{F}$, $f = ?$ $D = ?$

Ans: $f = 12\text{ kHz}$ $D = 66.67\%$

12. For an IC timer based astable multivibrator
given $D = 75\%$, $f = 1\text{ kHz}$ $R_2 = 3.6\text{ k}\Omega$
 $C = 0.1\text{ }\mu\text{F}$, calculate T_{ON} and R_1 .

Sol: given $D = 0.75$, $f = 1\text{ kHz}$ $R_2 = 3.6\text{ k}\Omega$,
 $C = 0.1\text{ }\mu\text{F}$.

$$\therefore T = \frac{1}{f} = \underline{\underline{1\text{ ms}}}$$

Scanned by CamScanner

Date

P	N	B
---	---	---

$$\text{Duty cycle} = \frac{T_{ON}}{T}$$

$$\therefore T_{ON} = D \times T$$

$$= 0.75 \times 1 \times 10^{-3}$$

$$= \underline{\underline{750\text{ }\mu\text{s}}}$$

$$T_{ON} = 0.693 (R_1 + R_2) C$$

$$750 \times 10^{-6} = 0.693 (R_1 + 3.6\text{ k}\Omega) 0.1 \times 10^{-6}$$

$$= 6.93 \times 10^{-8} R_1 + 2.4948 \times 10^{-4}$$

$$\therefore 750 \times 10^{-6} - 249.48 \times 10^{-6} = 6.93 \times 10^{-8} R_1$$

$$501 \times 10^{-6} = 6.93 \times 10^{-8} R_1$$

$$\therefore R_1 = 72.29 \times 100$$

$$= \underline{\underline{7.229\text{ k}\Omega}}$$

13. For an IC 555 timer, $D = 60\%$, $f = 2\text{ kHz}$

$R_2 = 3\text{ k}\Omega$, $C = 0.1\text{ }\mu\text{F}$. $R_1 = ?$

Solve the problem.

PROBLEMS ON IC 555 TIMER:

- 1) For an IC 555 timer, $T_{ON} = 3\text{sec}$, $T_{OFF} = 1\text{sec}$ and $C = 10\mu\text{F}$. Calculate the Value of R_1 and R_2 .

Solution:

$$\text{Given: } T_{ON} = 3\text{sec}, T_{OFF} = 1\text{sec}, C = 10\mu\text{F}$$

Solution:

$$T_{OFF} = 0.693 R_2 C$$

$$1 = 0.693 \times R_2 \times 10 \times 10^{-6}$$

$$R_2 = 144 \text{ K}\Omega$$

$$T_{ON} = 0.693(R_1 + R_2)C$$

$$\text{Therefore } R_1 = 288.6 \text{ K}\Omega$$

- 2) For an IC 555 timer, given $D = 75\%$, $f = 1 \text{ KHz}$, $R_2 = 3.6 \text{ k}\Omega$, $C = 0.1\mu\text{F}$. Calculate R_1 .

Solution:

$$\text{Given: } D = 75\% \Rightarrow 0.75$$

$$f = 1 \text{ kHz}, R_2 = 3.6 \text{ k}\Omega, C = 0.1\mu\text{F}$$

$$D = \frac{T_{ON}}{T}$$

$$T = \frac{1}{f} \Rightarrow 1 \text{ m sec}$$

$$T_{ON} = D \times T$$

$$T_{ON} = 0.75 \times 10^{-3} \text{ sec} = 750 \mu\text{sec}$$

$$T_{OFF} = 0.693 R_2 C$$

$$T_{OFF} = 249 \mu\text{sec}$$

Since $D > 50\%$, $T_{ON} > T_{OFF}$

$$T_{ON} = 0.693(R_1 + 3600)0.1 \times 10^{-6}$$

$$\text{Therefore } R_1 = 7.215 \text{ k}\Omega$$

Problems on RC oscillator:

1. In an RC phase shift oscillator, $R = 500\Omega$ and $C = 0.1\mu F$. Calculate the frequency of oscillations.

Solution:

Given $R = 500\Omega$, $C = 0.1\mu F$

Frequency of oscillations is given by

$$f = \frac{1}{2\pi RC\sqrt{6}}$$

$$f = \frac{1}{2\pi \times 500 \times 0.1 \times 10^{-6} \times \sqrt{6}}$$

$$\therefore f = 1.299\text{kHz}$$

2. In an RC phase shift oscillator, $R = 1000\Omega$. If the frequency of oscillations is 5kHz, calculate the value of C.

Solution:

Given $R = 1000\Omega$, $f = 5\text{kHz}$.

Frequency of oscillations is given by

$$f = \frac{1}{2\pi RC\sqrt{6}} \text{ or } C = \frac{1}{2\pi Rf\sqrt{6}}$$

$$\therefore C = \frac{1}{2\pi \times 1000 \times 5000\sqrt{6}}$$

$$C = 0.0129\mu F$$