

# PRASTHUTHI - CSE - E

(25)

## UNIT 1 BE - Answer Key:


MCA Page ① - 3 ②

80 Q's.


①

- ① Draw the VI characteristics for silicon and germanium diode and define the diode characteristic.

② Silicon diode:

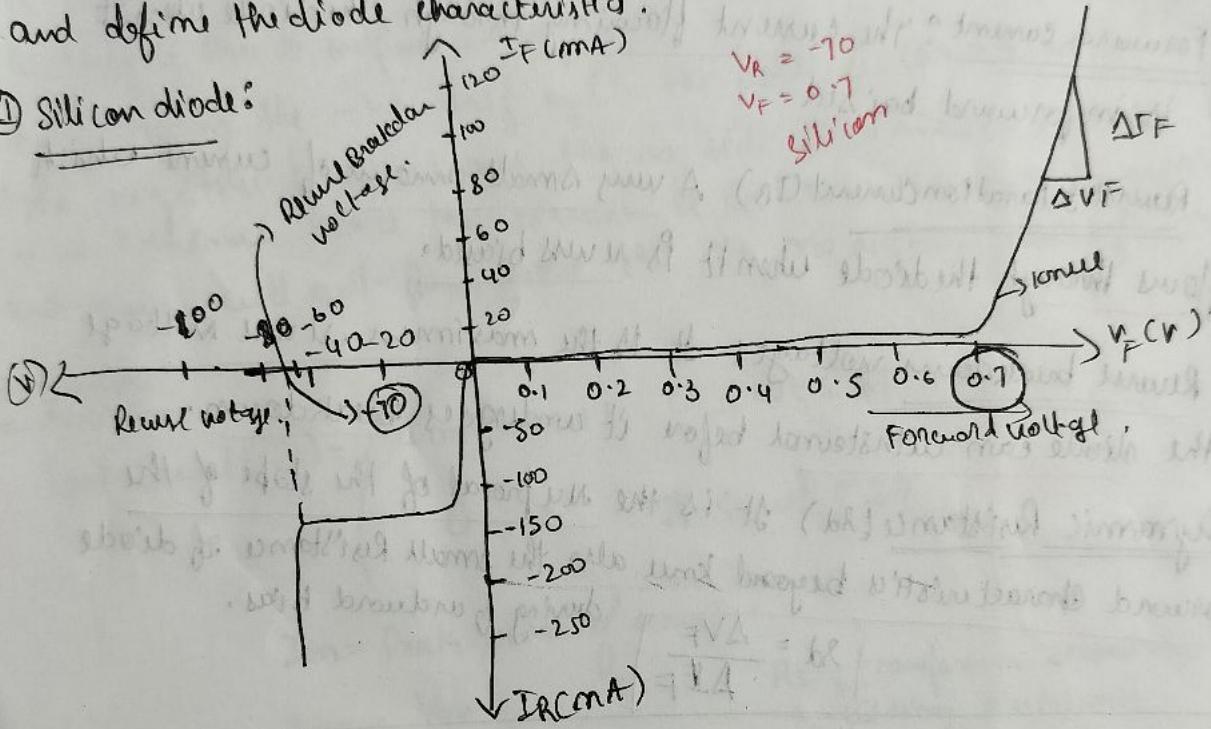

③ germanium Diode:

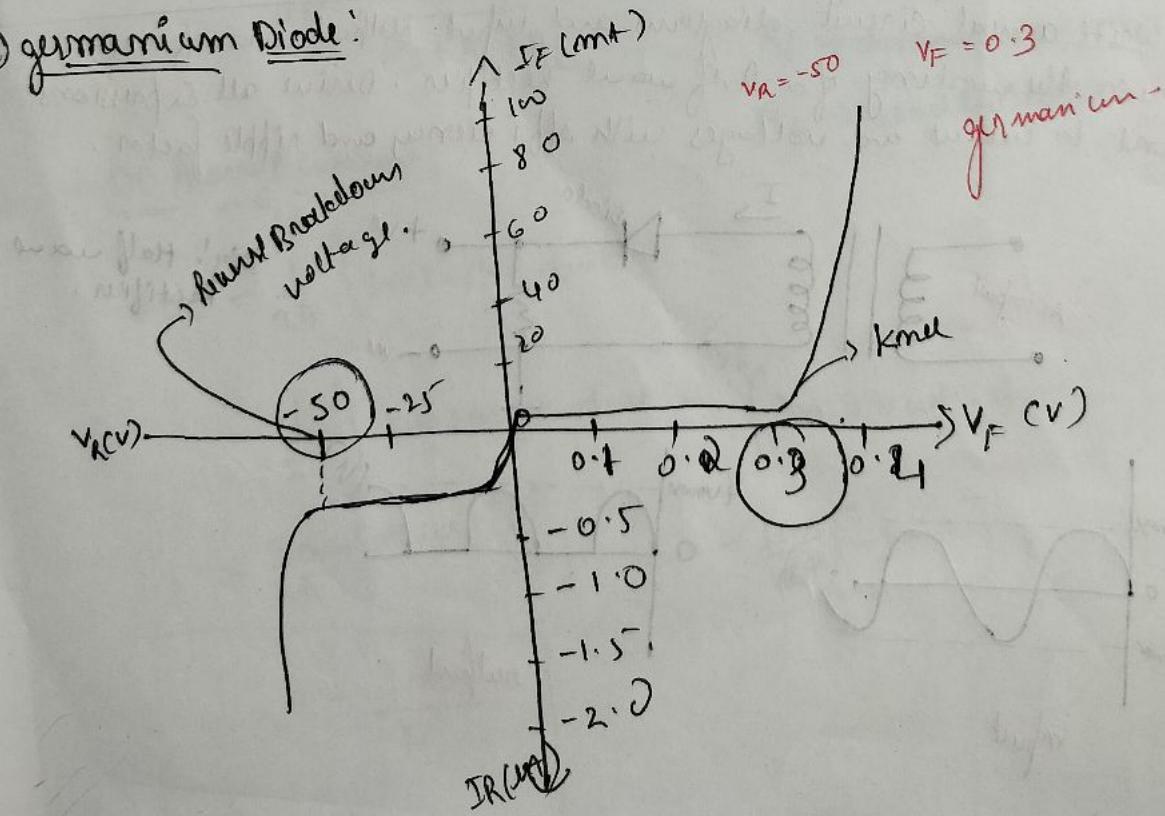



## Diode Characteristics:

(Knee voltage)

- ① Forward voltage ( $V_F$ ): The voltage drop across the diode when it is forward biased / conducting.
- ② Forward current: The current flowing through the diode when it is in forward bias.
- ③ Reverse saturation current ( $I_R$ ): A very small amount of current which flows through the diode when it is reverse biased.
- ④ Reverse breakdown voltage: It is the maximum reverse voltage the diode can withstand before it undergoes breakdown.
- ⑤ Dynamic Resistance ( $r_d$ ): It is the reciprocal of the slope of the forward characteristics beyond knee also the small resistance of diode during forward bias.

$$r_d = \frac{\Delta V_F}{\Delta I_F}$$

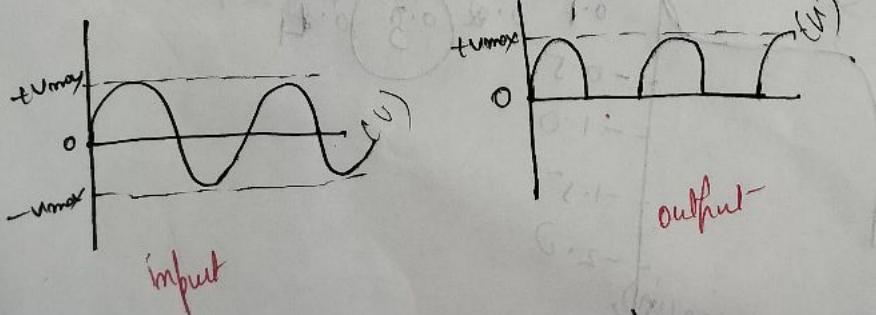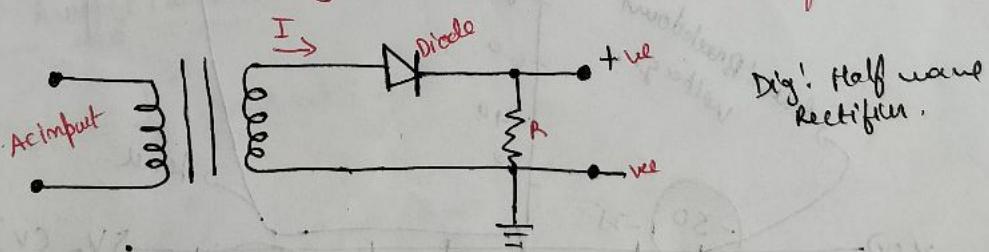- ② Write a neat circuit diagram and input output waveforms, Explain the working of a half wave rectifier. Derive all Expressions relevant to current and voltages with efficiency and ripple factor.



(2)

### Working:

During the +ve half cycle p-side is connected to the +ve terminal and m-side is connected to the negative terminal, hence the circuit is in forward biased condition, and current starts flowing through RL therefore this is output waveform.

Now, During the -ve half cycle the p-side is connected to the negative terminal and the m-side is connected to the +ve terminal hence the circuit is in reverse biased condition and current will not flow hence there is no output waveform(V).

### Expressions:

$$\text{load current } (I_L) = \begin{cases} I_{m \sin \omega t} & 0 \leq \omega t \leq \pi \\ 0 & \pi \leq \omega t \leq 2\pi \end{cases} \quad (1)$$

$I_m$  = Peak value of current.

$$I_m = \frac{V_m}{R_s + R_f + R_L}$$

$R_s$  = Transformer secondary winding Resistance.

$R_f$  = dynamo Resistance.

$R_L$  = Load Resistance.

$I_{DC} \Rightarrow$  DC Average current!

$$I_{DC} = \frac{1}{2\pi} \int_0^{2\pi} I_{m \sin \omega t} d\omega t$$

$$= \frac{1}{2\pi} \int_0^{\pi} I_{m \sin \omega t} d\omega t + \int_{\pi}^{2\pi} I_{m \sin \omega t} d\omega t$$

$$= \frac{I_m}{2\pi} [\cos \omega t]_0^{\pi} = -\frac{I_m}{2\pi} [(-1 - 1)] = \frac{I_m}{\pi}$$

$$I_{DC} = \frac{I_m}{\pi}$$

$V_{DC}$

$\Rightarrow$  DC Average Voltage.

$$V_{DC} = I_{DC} \cdot R_L$$

$$= \frac{I_{m\text{ rms}}}{\pi} \cdot \frac{R_L}{R_S + R_B + R_L}$$

$$= \frac{V_{m\text{ sinus}}}{R_S + R_B + R_L}$$

$$= \frac{I_{m\text{ rms}}}{\pi} \cdot R_L$$

$$= \frac{\cancel{R_L} V_m}{R_S + R_B + R_L} \cdot \frac{R_L}{\pi}$$

$$R_S \ll R_L$$

$$\boxed{V_{DC} = \frac{V_m}{\pi}}$$

$I_{rms}$

$$I_{rms} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} I_L^2 d\omega t}$$

$$= \sqrt{\frac{1}{2\pi} \int_0^{2\pi} I_{m\text{ rms}}^2 \sin^2 \omega t d\omega t}$$

$$= \sqrt{\frac{I_{m\text{ rms}}^2 \pi}{2\pi} \int_0^{2\pi} \frac{1 - 2 \cos \omega t}{2} d\omega t}$$

$$\boxed{I_{rms} = \frac{I_m}{2}}$$

$$V_{rms} = I_{rms} \cdot R_C$$

$$= \frac{V_m}{2}$$

### Ripple factor:

$$\lambda = \frac{I_{ac}}{I_{dc}}$$

$$I_{ac}^2 = I_{rms}^2 - I_{dc}^2$$

$$\lambda = \frac{\sqrt{I_{rms}^2 - I_{dc}^2}}{I_{dc}}$$

$$\lambda = \sqrt{\frac{I_{rms}^2}{I_{dc}^2}} - 1$$

$$I_{rms} = \frac{Im}{2}$$

$$I_{dc} = \frac{Im}{\pi}$$

$$\lambda = 1.21 = \underline{121\%}$$

### Efficiency:

$$\eta = \frac{P_{dc}}{P_{ac}}$$

$$P_{dc} = I_{dc}^2 \cdot R_L$$

$$P_{ac} = I_{rms}^2 [R_L + R_B + R_s]$$

$$\eta = \frac{I_{dc}^2 \cdot R_L}{I_{rms}^2 [R_L + R_B + R_s]}$$

$$I_{rms} = \frac{Im}{2}$$

$$I_{dc} = \frac{Im}{\pi}$$

$$\eta = 0.406$$

$$= \underline{40.6\%}$$



(6)

"athis"



④ (3) Write circuit diagrams and graphs explaining diode models!

Ans: The diode is a two terminal non-linear device whose VI characteristics are dependent on the polarity of applied voltage.



### ① Ideal Diode

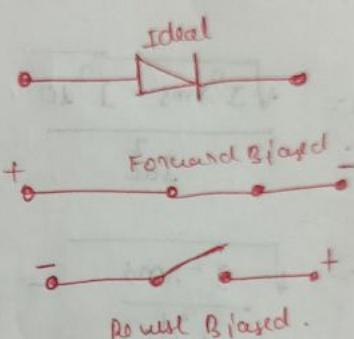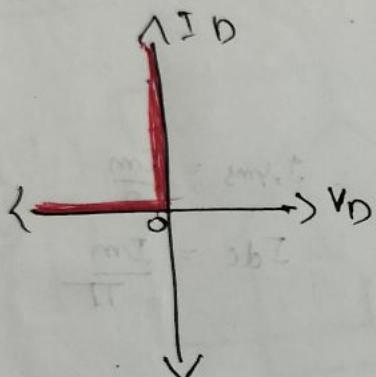

### ② Steady State Model


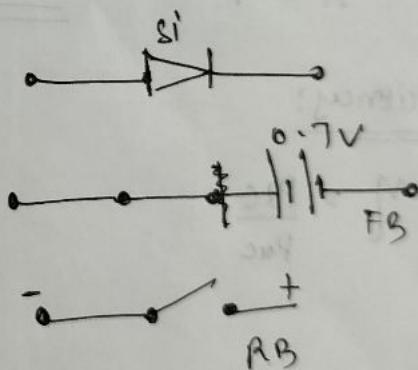
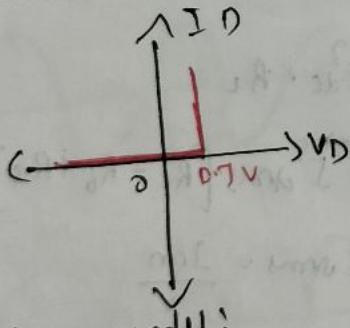


### ③ Piecewise Linear Model

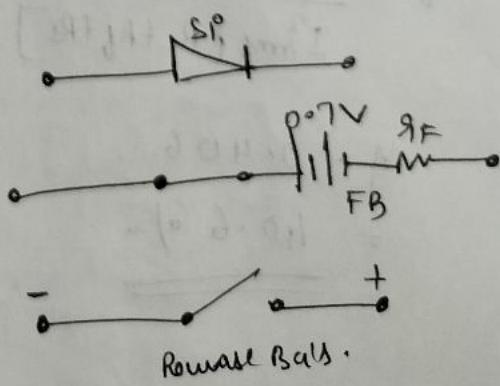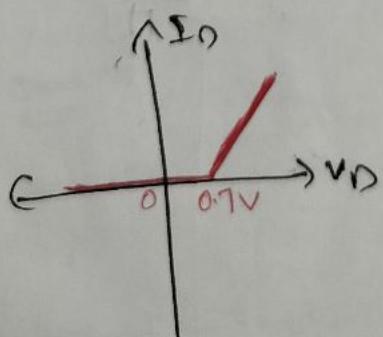

④ Write a neat circuit diagram and relevant graphs of input output waveforms to explain the working of a bridge Rectifier and derive all the expressions relevant to current, voltage, with efficiency and ripple factor. (14)

Ans! Bridge Rectifier

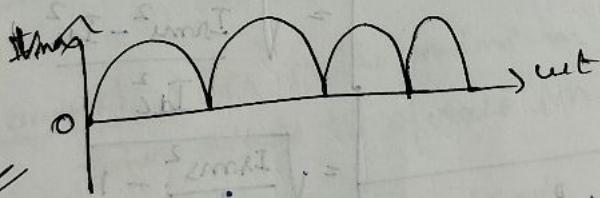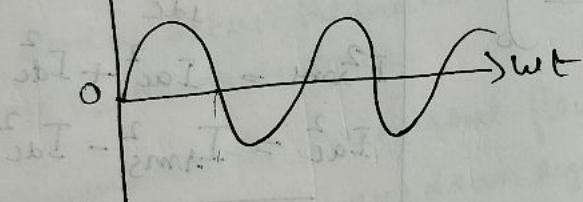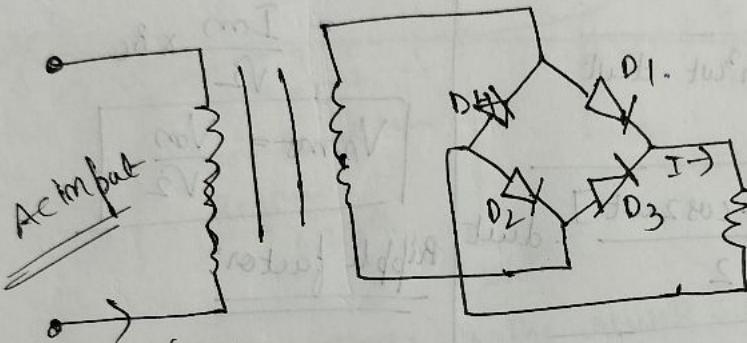

Derivation:

$$I_{DC} = \frac{1}{2\pi} \int_0^{2\pi} I_{ms \sinut. ult}$$

$$= \frac{1}{2\pi} \left[ I_{ms \sinut. ult} + \int_{\pi}^{2\pi} I_{ms \sinut. ult} \right]$$

$$I_{DC} = \frac{1}{2\pi} \left( \frac{1}{2} \int_{\pi}^{2\pi} I_{ms \sinut. ult} \right)$$

$$= \frac{1}{\pi} \int_{\pi}^{2\pi} I_{ms \sinut. ult}$$

$$\Rightarrow I_{DC} = \frac{Im}{\pi} [-\cos ut]_0^{\pi}$$

$$= -\frac{Im}{\pi} [1 - 1]$$

$$I_{DC} = \frac{2Im}{\pi}$$

DC voltage

$$V_{DC} = I_{DC} \cdot R_L \\ = 2 \frac{I_m}{\pi} \cdot R_L = I_m = \frac{V_m}{R_s + R_b + R_L} \Rightarrow V_{DC} = \frac{2V_m}{\pi}$$

$I_{rms}$

$$I_{rms} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} I_L^2 \cdot dwt} \\ = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} I_m^2 \sin^2 wt \cdot dwt} \\ = \sqrt{\frac{I_m^2 \pi}{\pi} \int_0^{2\pi} \left[ \frac{1 - \cos 2wt}{2} \right] \cdot dwt} \\ = \sqrt{\frac{I_m^2}{2\pi} \left[ wt - \frac{\sin 2wt}{2} \right]_0^\pi} \\ = \sqrt{\frac{I_m^2}{2}} \\ \boxed{I_{rms} = \frac{I_m}{\sqrt{2}}}$$

Norms:  $I_{rms} \times R_L$

$$= \frac{I_m}{\sqrt{2}} \times R_L$$

$$\boxed{V_{rms} = \frac{V_m}{\sqrt{2}}}$$

Ripple factor:

$$\lambda = \frac{I_{ac}}{I_{dc}}$$

$$I_{rms}^2 = I_{ac}^2 + I_{dc}^2$$

$$I_{ac}^2 = I_{rms}^2 - I_{dc}^2$$

$$= \sqrt{\frac{I_{rms}^2 - I_{dc}^2}{I_{dc}^2}}$$

$$= \sqrt{\frac{I_{rms}^2}{I_{dc}^2} - 1}$$

$$= \sqrt{\frac{I_m^2/2}{4I_m^2/\pi^2} - 1}$$

$$= \sqrt{\frac{\pi^2}{8} - 1} \\ = 0.483$$

$$\lambda \cdot 100 = \frac{48.3}{100} \text{ of DC component}$$

$$\eta = \text{Efficiency} = \frac{P_{dc}}{P_{ac}} = \frac{I_{dc}^2 \cdot R_L}{I_{rms}^2 (R_s + 2R_b + R_L)}$$

$$I_{dc} = 2 \frac{I_m}{\pi} \quad I_{rms} = \frac{I_m}{\sqrt{2}}$$


$$\eta = \frac{4I_m^2}{\pi^2} \cdot R_L = \frac{8}{\pi^2} \times \left( \frac{1}{1 + \left( \frac{R_s + 2R_b}{R_L} \right)} \right)$$

$$\frac{I_m^2}{2} (R_s + 2R_b + R_L)$$

$$\eta = \frac{8}{\pi^2} = 0.812 \quad \boxed{\eta = 81.2\%}$$

Questionbank

5) Equivalent circuit  $\Rightarrow$

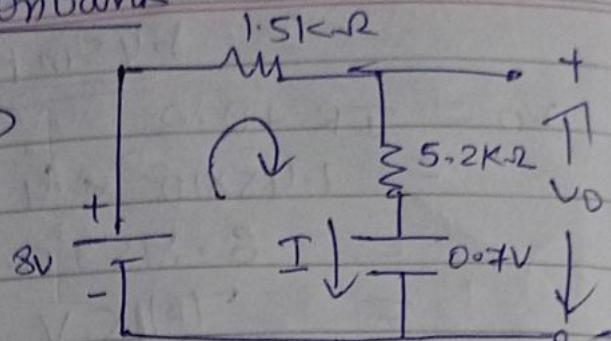

by applying KVL,

$$8V - 1.5I \times 10^3 - 5.2 \times 10^3 I - 0.7 = 0$$

$$\Rightarrow 8 - 6.7 \times 10^3 I - 0.7 = 0$$

$$-6.7 \times 10^3 I = 0.7 - 8$$

$$I = \frac{-1.3}{-6.7 \times 10^3}$$

$$= 1.08 \times 10^{-3}$$

$$I = \underline{\underline{1.08mA}}$$


$$V_o = I \times R + 0.7$$

$$= 1.08 \times 10^{-3} \times 5.2 \times 10^3 + 0.7$$

$$= 5.616 + 0.7$$

$$= \underline{\underline{6.316V}}$$

6) Equivalent circuit  $\Rightarrow$

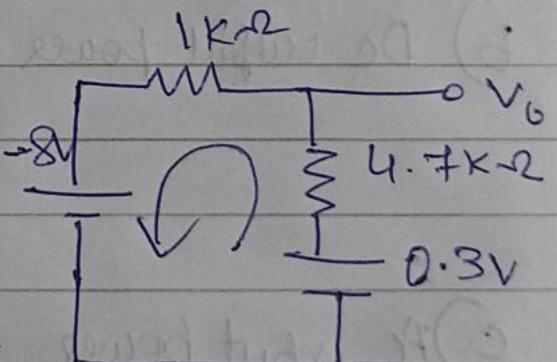

by applying KVL,

$$-(-8) + 1 \times 10^3 I + 4.7 \times 10^3 I$$

$$+ 0.3 = 0$$

$$-8 - 5.7 I \times 10^3 = -0.3$$

$$I = \frac{0.3 + 8 \times 10^{-3}}{5.7} + \text{ignore -ve sign}$$

$$32 - 25 \text{ mA} \times R_S - 24 = 0$$

$$\therefore R_S = \frac{32V - 24V}{25 \text{ mA}} \\ = \underline{\underline{320 \Omega}}$$

ii)  $I_2 = I_S - I_L$

$$I_L = \frac{V_2}{R_L} = \frac{24}{1200} = 20 \text{ mA}$$

$$I_2 = 25 \text{ mA} - 20 \text{ mA} \\ = \underline{\underline{5 \text{ mA}}}$$

12)  $V_2 = 12V, P_2 = 360 \text{ mW}, V_S = 24V$

i)  $I_L = 0, I_S = I_{2\max}$   
 $P_2 = I_2 V_2$

$$I_2 = \frac{V_2}{R_2} = \frac{12}{360} \approx \frac{P_2}{V_2} = \frac{360}{12} = 30 \text{ mA} \\ I_2 = I_S$$

Applying KVL,  $V_S - I_S R_S - V_2 = 0$ .  
 (Formula)  
 $24 - 30 \times R_S - 12 = 0$

$$R_S = \frac{24 - 12}{30} = \frac{12}{30 \times 10^3} \\ = 0.4 \times 10^3 = \underline{\underline{400 \Omega}}$$

ii)  $I_2 = I_S - I_L \rightarrow ①$

$$I_L = \frac{V_2}{R_L} = \frac{12}{1200} = \underline{\underline{9.6 \text{ mA}}}$$

①  $\Rightarrow I_2 = 30 - 9.6 = \underline{\underline{20.4 \text{ mA}}}$

$$= \underline{1.45mA}$$

$$V_o = IR + 0.3$$

$$= 1.45 \times 10^3 \times 4.7 \times 10^3 + 0.3$$

$$= 6.815 + 0.3$$

$$= \underline{\underline{7.115V}}$$

7) Given,  $V_m = 40V$ ,  $f = 50Hz$ ,  $R_L = 1k\Omega$ ,  $R_F = 8\Omega$

a) peak value of load current,

$$I_m = \frac{V_m}{R_L + R_F} = \frac{40}{1 \times 10^3 + 8} = \frac{40}{1008} =$$

$$= 0.0396 = \underline{39.6mA}$$

$$I_{dc} = \frac{I_m}{\pi} = \frac{39.6}{3.14} = \underline{\underline{12.6mA}}$$

$$I_{rms} = \frac{I_m}{2} = \frac{39.6}{2} = \underline{19.8mA}$$

b) Dc output power,  $P_{dc} = I_{dc}^2 \times R_L$

$$= (12.6)^2 \times 1 \times 10^3 \times 10^3 \times 10^{-3}$$

$$= 158.76 \times 10^3 W$$

$$= \underline{158.76mW}$$

c) Ac input power,  $P_{ac} = I_{rms}^2 (R_L + R_F)$

$$= (19.8 \times 10^{-3})^2 (1000 + 8)$$

$$= 392.04 \times 1008$$

$$= 395176.32 \times 10^{-6}$$

$$= 395.17 \times 10^{-3} W$$

$$= \underline{395.17mW}$$

d) efficiency,  $\eta = \frac{P_{dc}}{P_{ac}} = \frac{158.76 \text{ mW}}{395.17 \text{ mW}}$   
 $= 0.4017$   
 $\therefore \eta = \underline{\underline{40.17\%}}$

8) Given,  $V_{2rms} = 110 \text{ V}$ ,  $R_f = 25 \Omega$ ,  $R_L = 1 \text{ k}\Omega$ .

$$V_{2rms} = \frac{V_m}{\sqrt{2}} \Rightarrow V_m = V_{2rms} \times \sqrt{2} = 155.56 \text{ V}$$

i)  $I_m = \frac{V_m}{2R_f + R_L} = \frac{155.56}{50 + 1 \times 1000} = \underline{\underline{148.15 \text{ mA}}}$

ii)  $I_{dc} = \frac{2I_m}{\pi} = \frac{2 \times 148.15 \text{ mA}}{\pi} = 94.36 \text{ mA}$

iii)  $V_{dc} = I_{dc} \times R_L = 94.36 \text{ mA} \times 1 \text{ k}\Omega = \underline{\underline{94.36 \text{ V}}}$

10)  $P_2 = 600 \text{ mW}$

Apply KVL,

$$32 - I_s R_s - 24 = 0 \quad \textcircled{1}$$

without load,


$$I_L = 0, \text{ for } R_L = 0$$

$$I_S = I_Z + I_L, \quad I_L = 0, \quad I_S = I_{Zmax}$$

$$P_2 = I_Z V_2$$

$$I_Z = \frac{P_2}{V_2} = \frac{600 \text{ mW}}{24 \text{ V}} = \underline{\underline{25 \text{ mA}}} = I_S$$


Substituting in \textcircled{1}.

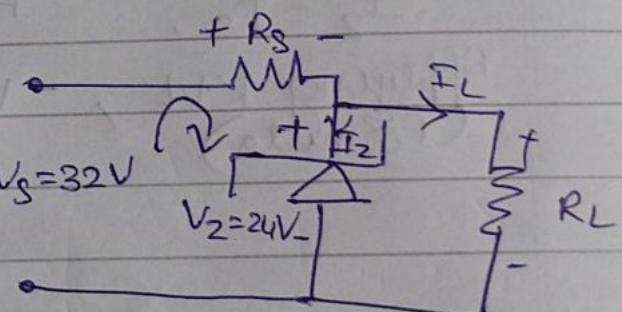

5/6, 7, 8

9, 13, 14, 15, 16 (5)

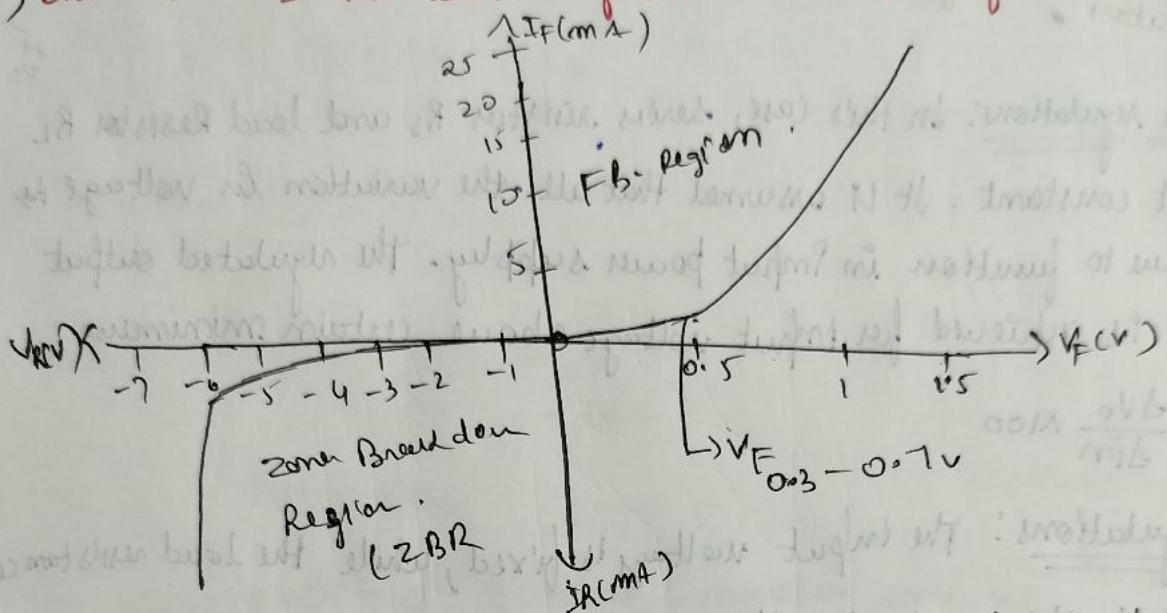Q) Draw the V-I characteristics of a zener diode and define zener parameters.



① zener Breakdown voltage: is the reverse-bias voltage at which the device enters the breakdown region, maintaining a constant voltage  $V_2$  across the device.

② zener-current (= the current that flows through the diode when it is in the breakdown region).

③ knee current: This is the minimum current required for the zener diode to operate in the breakdown.

④ ZBR: It is where the diode starts conducting a large current while maintaining a nearly constant voltage across it.

Ans  
9/P

$$0.7 + 3I = 31$$

$$0.7 + 3I = 31$$

$$(0.7 + 3I) \cdot 200 = 31$$

13) Define Line Regulation and Load Regulation in zener voltage regulation.

Ans: Line Regulation: In this case, series resistor  $R_s$  and load resistor  $R_L$  are kept constant. It is assumed that all the variation in voltage is due to fluctuation in input power supply. The regulated output voltage  $V_o$  is achieved for input voltage above certain minimum level  $\frac{V_o}{\alpha_{min}} \approx 100$

Load Regulation: The input voltage is fixed, while the load resistance is varied. The constant output voltage is obtained as long as the load resistance  $R_L$  is maintained above a minimum level.

$$\frac{V_{oL} - V_{oN}}{V_{oL}} \approx 100$$

14) Bring out the relationship b/w the transistor current gains  $\alpha$  and  $\beta$ .

$$I_E = I_B + I_C \quad \text{--- (1)}$$

$\downarrow$        $\hookrightarrow$  collector current  
Emitter current      base current

The ratio of collector current to emitter current is called  $\alpha$  [common base gain]

$$\alpha_{dc} = \frac{I_C}{I_E} \quad \text{--- (2)}$$

The ratio of collector current to base current is called  $\beta$  [common emitter gain]

$$I_E = I_C + I_B$$

$$I_C = I_E - \alpha_{dc}$$

$$\therefore I_C = \alpha_{dc}(I_E + I_B)$$

14) continue

6

$$I_C = \frac{ddc}{1-ddc} \cdot I_B$$

३

$$\text{Faither } \beta_{dc} = \frac{\beta_c}{\beta_B}$$

$$\therefore \beta_{dc} = \frac{\frac{dc}{E_B}}{1 - dc}$$



$$\therefore \text{Pac} \rightarrow \underline{\text{oldc}}$$

The relationships of  $\alpha$  and  $B$  parameters shall be

$$\beta = \frac{\alpha}{1-\alpha} \quad \text{and} \quad \alpha = \frac{\beta}{1+\beta}$$

15) Write neat circuit diagram explain the CB configuration of BJT and draw the input/output characteristics.

Ans: CB config BST

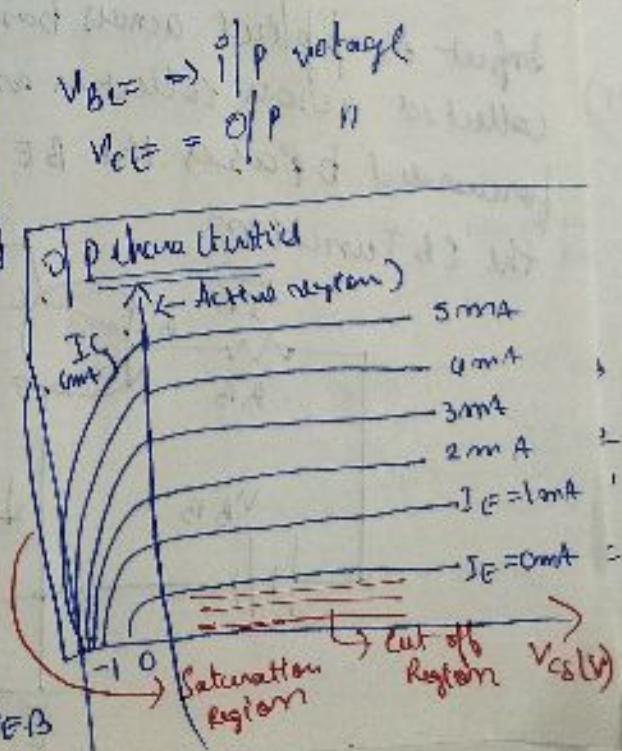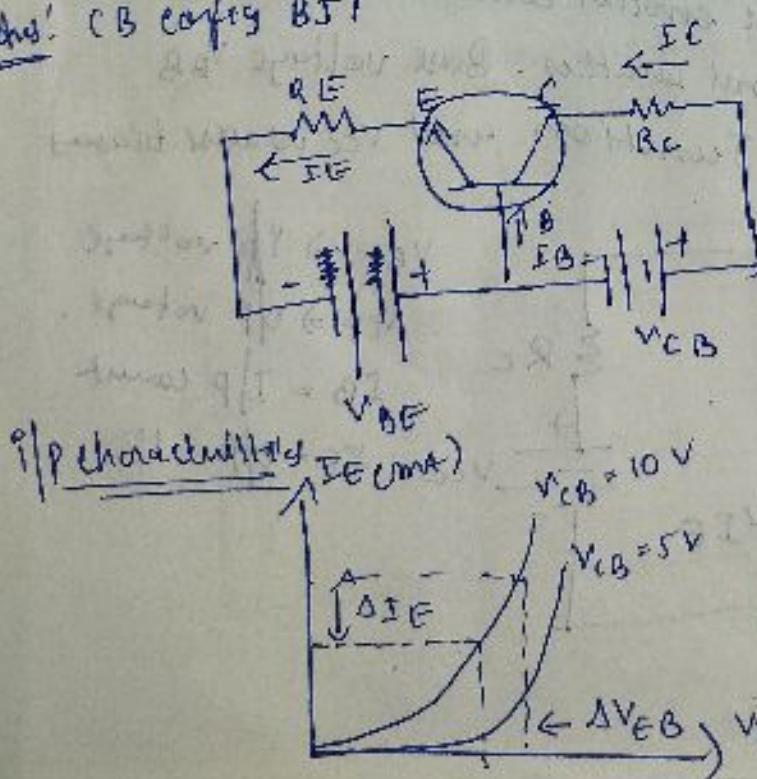

## Explanations:

The Base connection is common to both the input signal and the output signal too, with the output signal being applied between the base and the emitter terminals. Output is measured between the base and collector terminals.

→ Input characteristics is the curve b/w IE and Input voltage  $V_{EB}$  for constant collector base voltage  $V_{CB}$ .


→ After cut in voltage IE increases draughtily with small increase in  $V_{EB}$ .

→ As  $V_{CB}$  increases slight increase in IE is observed.

This is due to change in the width of the depletion charge.

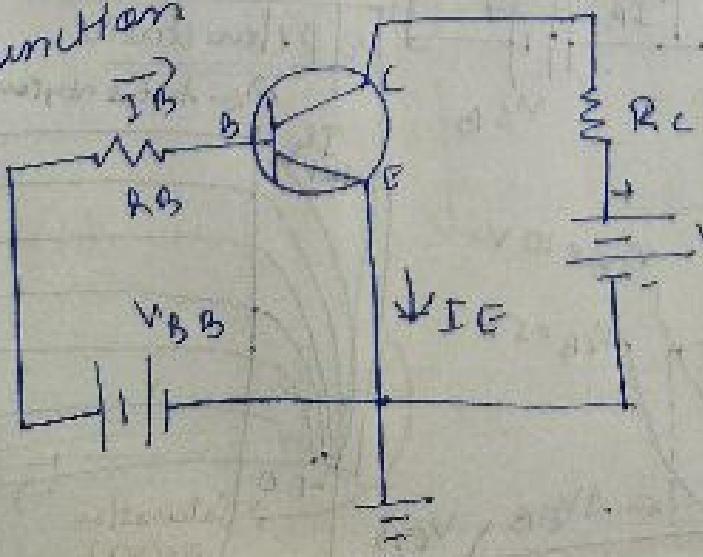(b) with neat circuit diagrams explain the CE configuration of BJT and draw its IP/OP characteristics.

Input is applied across base emitter terminal without biasing. Collector current  $I_C$  is forwarded to pass the BE junction and  $V_{CE}$  reverse biases the CB junction.





$$V_{BE} \rightarrow I/P \text{ voltage}$$

$$V_{CE} \rightarrow O/P \text{ voltage}$$


$$I_B = I/P \text{ current}$$

$$I_C = O/P \text{ "}$$

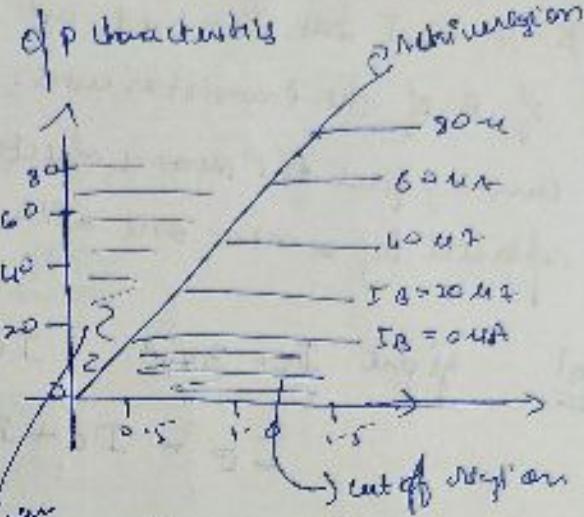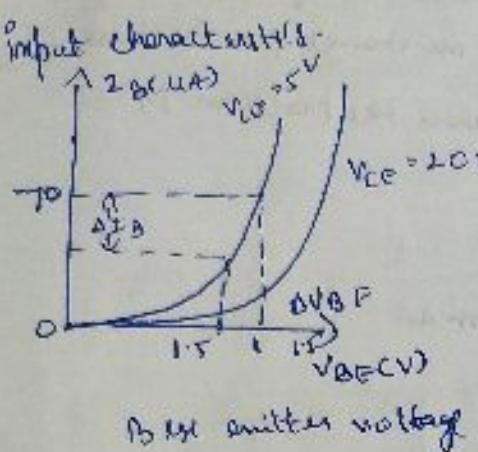


Transistor is in cut-off & that is no collector current, the LED does not emit when  $V_{CE}$  wave goes to high level, the transistor saturates. That's why the LED is collector current flows through the LED & emits bright light. Thus, LED is on for 1 sec & off for 1 sec.

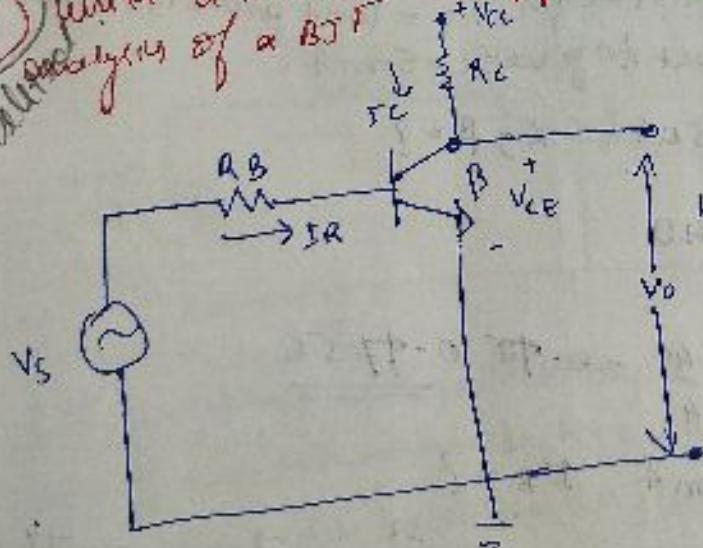(F) Write a neat circuit figure and graph, show the DC load line analysis of a BJT



$$V_{CE} = I_C R_C + V_{CE}$$

$$\therefore V_{CE} = V_{CC} - I_C R_C$$

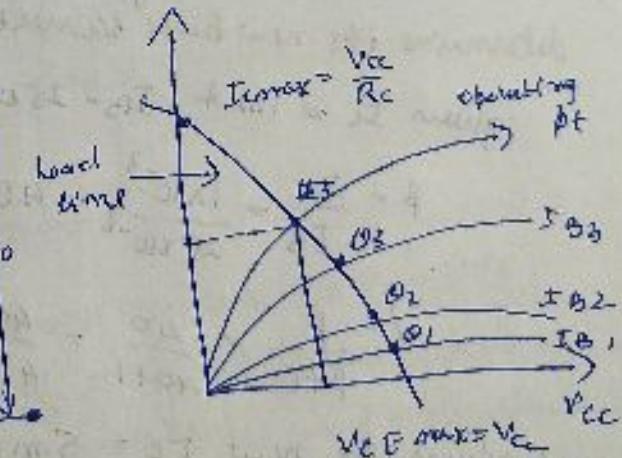

18) A BJT has  $I_C = 3\text{mA}$  and  $I_E = 3.03\text{mA}$ . Compute the value of  $\beta$  of the transistor used. Assuming no change in the base current, find the new collector current when the transistor is replaced by a new one with  $\beta$  of 70.

Ans) Given  $I_C = 3\text{mA}$      $I_E = 3.03\text{mA}$

$$I_E = I_C + I_B$$

$$I_B = 3.03 - 3 = \underline{\underline{0.03\text{mA}}}$$

$$\beta = \frac{I_C}{I_B} = \frac{3 \times 10^{-3}}{0.03 \times 10^{-3}} = \frac{300}{3} = \underline{\underline{100}}$$

To find new collector current when  $\beta = 70$

$$I_C = \beta \times I_B = 70 \times 0.03 \times 10^{-3} = \underline{\underline{2.1\text{mA}}}$$

19) Determine base  $\beta$  of transistor for  $I_C = 1\text{mA}$  and  $I_B = 25\mu\text{A}$  determine the new base current to give  $I_C = 5\text{mA}$ .

Given  $I_C = 1\text{mA}$      $I_B = 25\mu\text{A}$     &  $\beta = ?$

$$\beta = \frac{I_C}{I_B} = \frac{1 \times 10^{-3}}{25 \times 10^{-6}} = 40$$

$$\kappa = \frac{\beta}{\beta+1} = \frac{40}{40+1} = \frac{40}{41} = \underline{\underline{0.9756}}$$

now given the new  $I_C = 5\text{mA}$      $I_B = ?$

$$\beta = \frac{I_C}{I_B} \quad I_B = \frac{I_C}{\beta} = \frac{5 \times 10^{-3}}{40} = \frac{1 \times 10^{-3}}{8} = \frac{1.25 \times 10^{-4}}{8} = \underline{\underline{0.125\text{mA}}} \\ = \underline{\underline{125\mu\text{A}}}$$

Q) Calculate  $\alpha$ ,  $\beta$  and  $I_B$  of transistor that has  $I_C = 2.5 \text{ mA}$  and  $I_E = 2.55 \text{ mA}$

$$I_C = 2.5 \text{ mA} \quad I_E = 2.55 \text{ mA} \quad \alpha, \beta, I_B = ?$$


$$\alpha = \frac{I_C}{I_E} = \frac{2.5 \times 10^{-3}}{2.55 \times 10^{-3}} = 0.9804$$

$$\beta = \frac{\alpha}{1-\alpha} = \frac{0.9804}{1-0.9804} \Rightarrow 50.0$$

$$\text{now } \beta = \frac{I_C}{I_B}$$

$$I_B = \frac{I_C}{\beta} = \frac{2.5 \times 10^{-3}}{50} = 5 \times 10^{-5} = 0.05 \text{ mA}$$

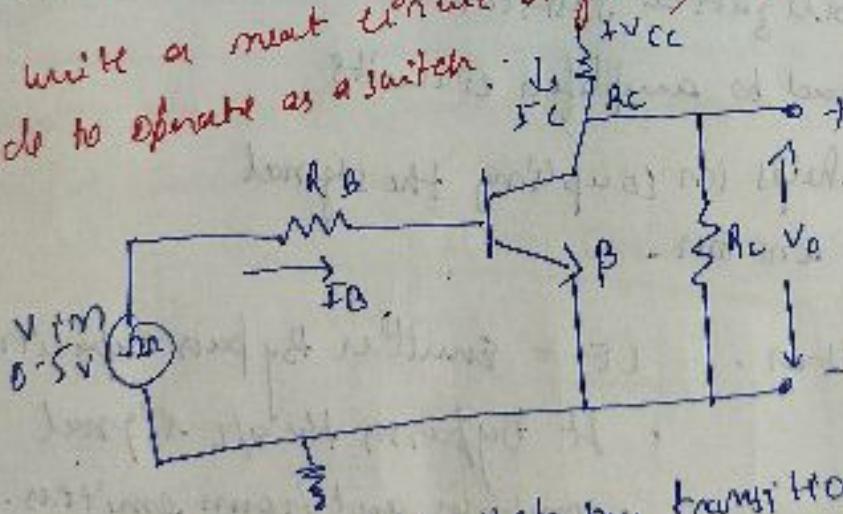~~Q) Dotted  
Same as 17~~  
2) Write a neat circuit diagram, explain how BJT can be made to operate as a switch.




A BJT functions as a switch by transitioning b/w two states: cut-off and saturation. In the cut-off no current flows, while in saturation, the base-emitter junction is forward-biased allowing current flow b/w collector and emitter.

23) Write a neat circuit diagram of a CE-RC coupled amplifier.

(i) Describe the significance of each component in the circuit.

(ii) Illustrate the phase reversal.

(iii) Draw the input output waveforms.

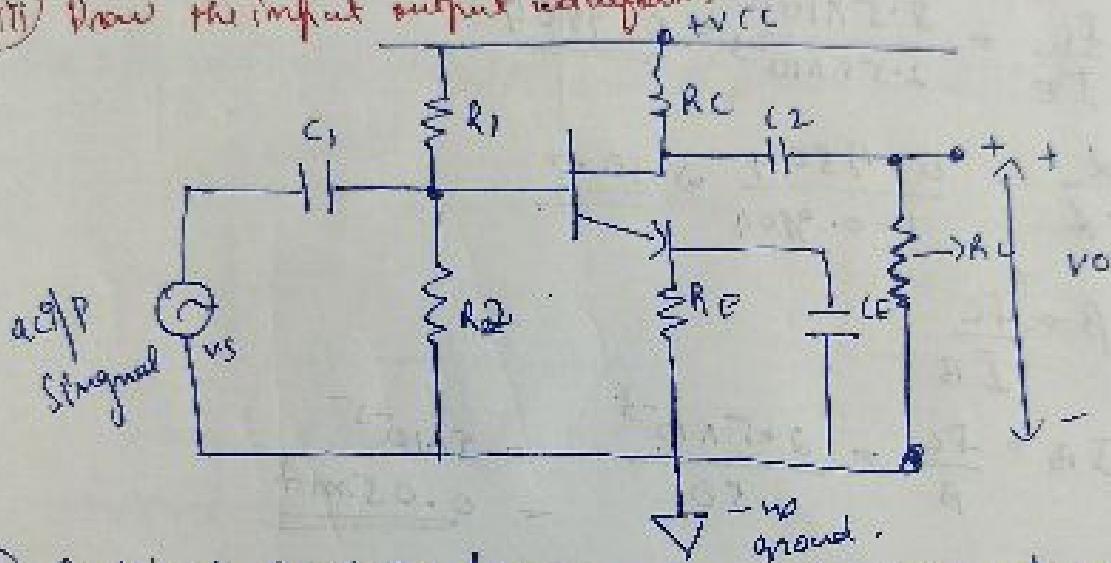

i) Resistors  $R_1$  &  $R_2$  form a voltage divider network for amplification.

- $R_E$  is emitter stabilizing resistor.

- $R_C$  serves as ac load to amplifier circuit.


- Capacitors  $C_1$  &  $C_2$  helps for coupling the signal from one stage to another.

- $C_1$  = Input capacitor. ( $E$  = Emitter bypass capacitor.)  
 $C_2$  = Output " . It bypasses the ac signal coming out from emitter.

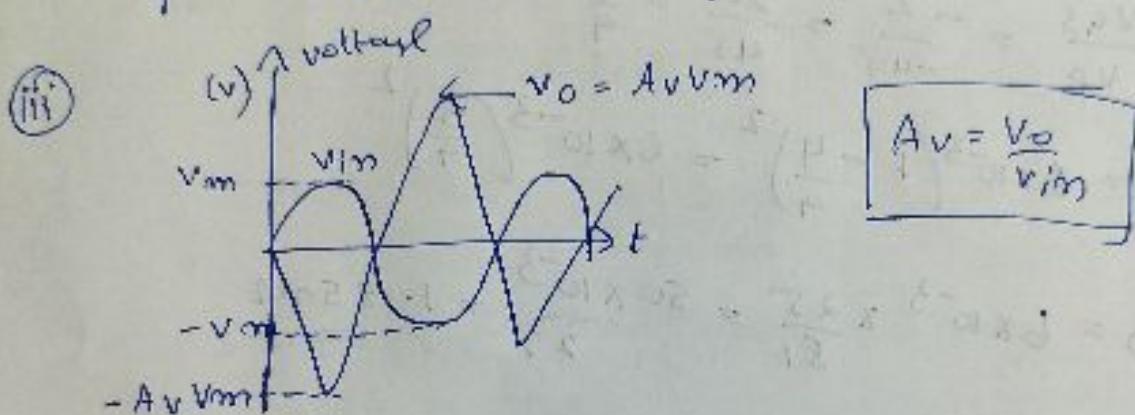ii) Phase reversal: when  $V_m$  is applied,  $I_B$  &  $I_C$  during the half cycle. Hence  $I_C = \beta I_B$  also.  $\therefore$


- During one half cycle base current  $I_B$ , hence collector terminal of transistor cut-ground.

- The O/P voltage is therefore collector to emitter voltage according to dc condn  $V_{CE} = V_{CC} - I_C (R_C + R_E)$
- If  $I_C \propto P$ ,  $V_{CE} \downarrow \propto$  with  $P \propto$
- When base current  $\uparrow$   $I_C \propto P \propto V_{CE} \uparrow$
- The O/P voltage is  $180^\circ$  out of phase with P/P




~~(24) D.R.K~~ ~~(25) D.R.K~~ ~~(26) D.R.K~~

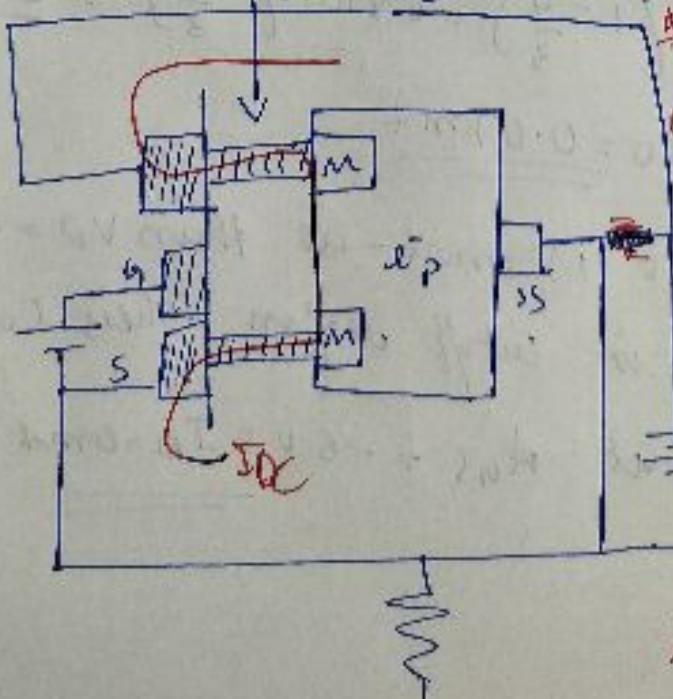25) write the neat connection diagrams, explain the drain and transfer characteristics of n-channel enhancement type MOSFET in  $SiO_2$  [leave bias point]



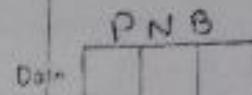Ans: Drain current will be zero for the  $V_{GS}$  is greater or equal to  $V_{TH}$  for the N-channel enhancement type mosfet. The transfer characteristic of N-channel enhancement type mosfet is + drain b/w  $V_{GS}$  and  $I_D$ .   
 $V_{DD}$  the transfer characteristic will always be in the region and zero till  $(V_{GS} = V_{TH})$ .




## CMOS Inverter

(2)

Q CMOS  $\rightarrow$  Complementary MOS, It uses 2 MOSFETs & E-MOSFETs for its construction.

A p-channel and n-channel E-MOSFETs when placed on the same substrate, it is known as Complementary MOS.

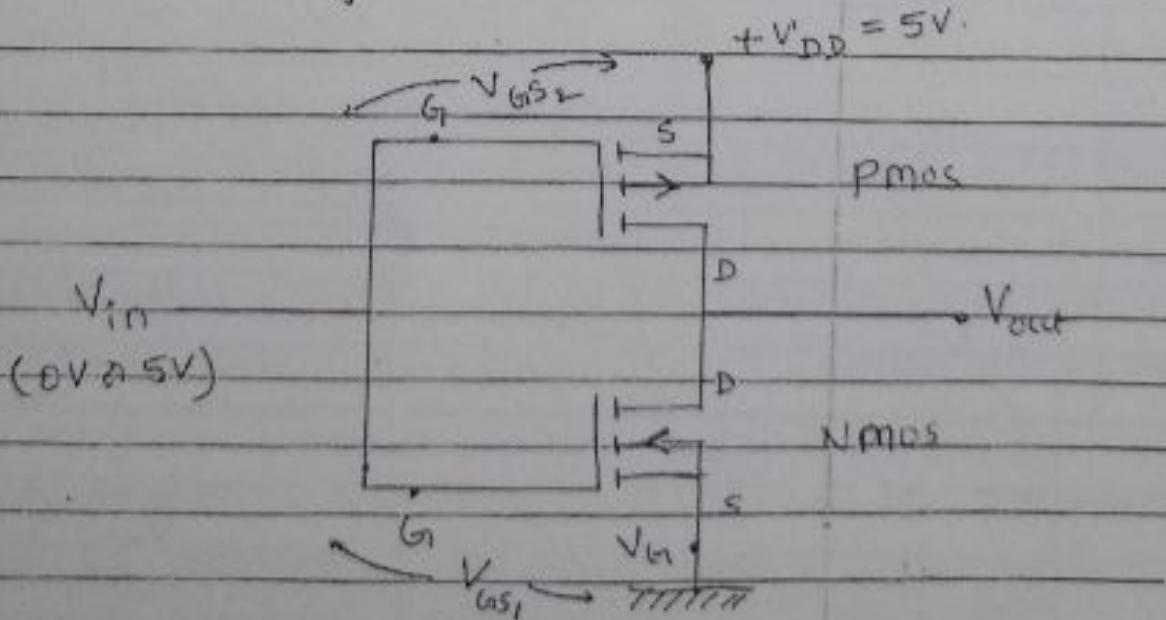- + It has low input impedance, fast switching speeds and less power consumption.
- + It is used in computer logic design.
- + one n-type mos (Nmos) and one p-type mos (Pmos) are connected in pairs to form CMOS.
- + Gates of the 2 devices are connected to form input terminals and 2 drain terminals are connected together to form output terminal, as shown in figure a) below.



What makes you happy? Fig a) CMOS inverter. # HappyCollegeDays